

ECE260B Winter 22

Clock Domain Crossing



Prof. Mingu Kang

UCSD Computer Engineering

Announcement

- **Lecture recording:** in Media Gallery
- **Upcoming HW this week:** deadline March 1st 1pm (Tuesday)
- **Midterm Announcement:** during Thursday lecture (17th)
- **TA will generate a project team randomly this week** if you haven't done so

  Clock Domain Crossing (Asynchronous Interface)



Examples of asynchronous interfaces


■ Asynchronous interface

- Interface between two or more modules operating with independent clocks
- Async interface helps independent operation of modules (e.g., freq. modulation)
- Even in a single core, many modules operate on its own clock domain
- Also, helps timing closure during P.D
- Though the freq. is identical, if the clock is independent, it is async interface
- Despite the source is common, the clock tree is different, it is safe to treat as async.

Synchronous Interface Solutions


- **Synchronizer**
 - minimize the meta stability at async. interface
 - often used when a single bit is delivered
- **Hand shaking protocol**
 - used to deliver multiple bits through async. interface
- **FIFO**
 - multi-bit support + fast

Meta-Stability at Async Interface

 





- The timing of input w.r.t. the receiving clock is completely random at async interface
- No guarantee that set-up time requirement is met
- Thus, meta-stability can happen

Synchronizer

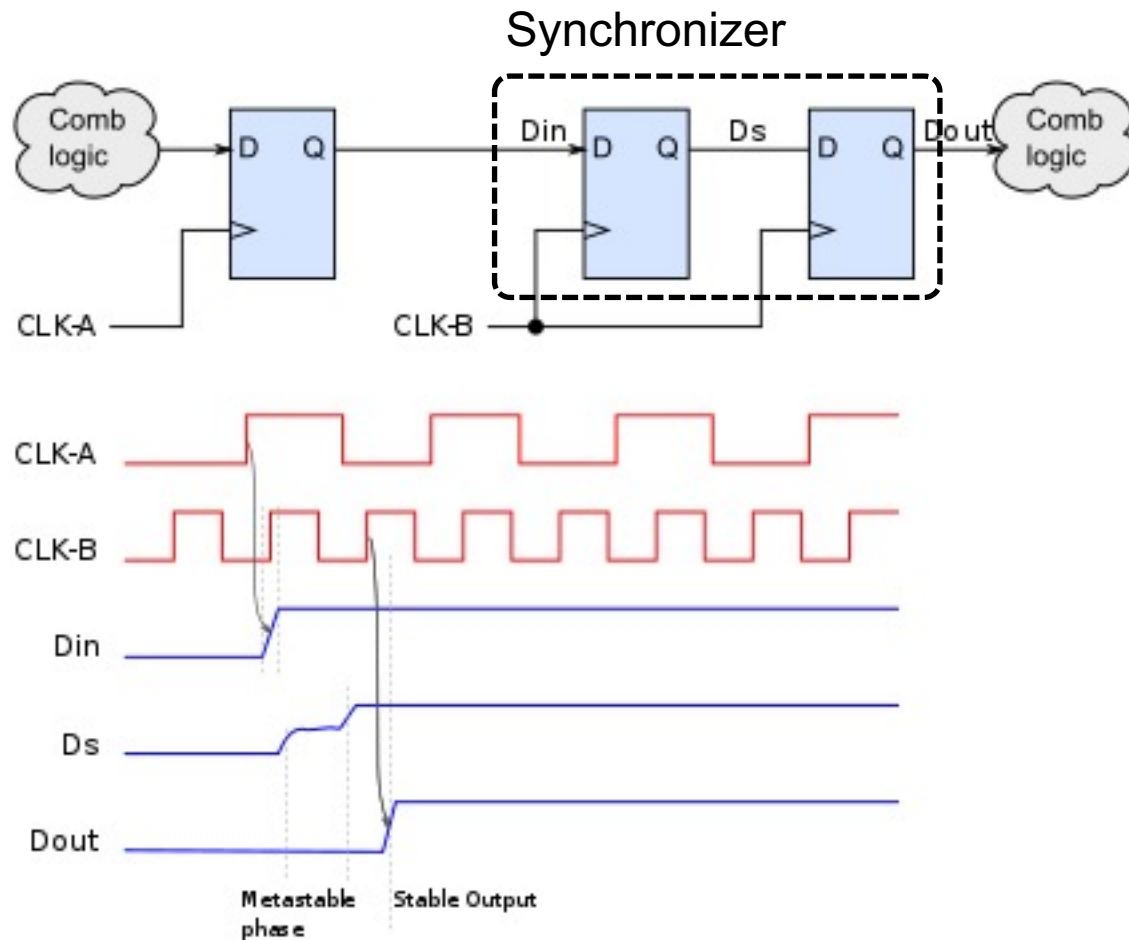

- Synchronizer: closely located 2 or 3 flip flop (FF)s
- 2nd FF's output are either 0 or 1 with high probability
- Combinational logic is protected from meta stable data
- Three FFs provides better stability
- Special STD cells are often provided by PDK

Timing Uncertainty in Synchronizer

    

Fail to flip data due to meta-stability

But, flipped in the next cycle

- For this nature, cycle-accurate timing prediction is difficult at the async interface

Synchronizer Implementation

```

module sync (in, clk, out);
  input in, clk;
  output reg out;

  reg int_q;
  always @ (posedge clk) begin
    int_q <= in;
    out <= int_q;
  end
endmodule

```

*Behavioral code
for synchronizer*

```

module top( ... )

  wire data_clk1;
  wire data_clk2;

  sync sync_instance (
    .in(data_clk1),
    .clk(clk2),
    .out(data_clk2)
  );
  ...

```

*Top module
during behavioral sim*



```

module top( ... )

  wire data_clk1;
  wire data_clk2;


  SDFQ1MA10TR sync_inst(
    .in(data_clk1),
    .clk(clk1),
    .out(data_clk2)
  );
  ...

```

*Top module
for tape-out*


- SDFQ1MA10TR: special STD cell to maximize the MTTF (mean-time-to-failure) by meta-stability

Synchronizer Failure

 


- Synchronizer is a good solution to deliver a single bit data from slow to fast domain crossing
- Not a good solution from fast to slow clock as pulse can be missing as above
- Also, not suitable to deliver multi-bit due to many FFs due to the **timing uncertainty between the data bits**



Hand Shaking Protocol

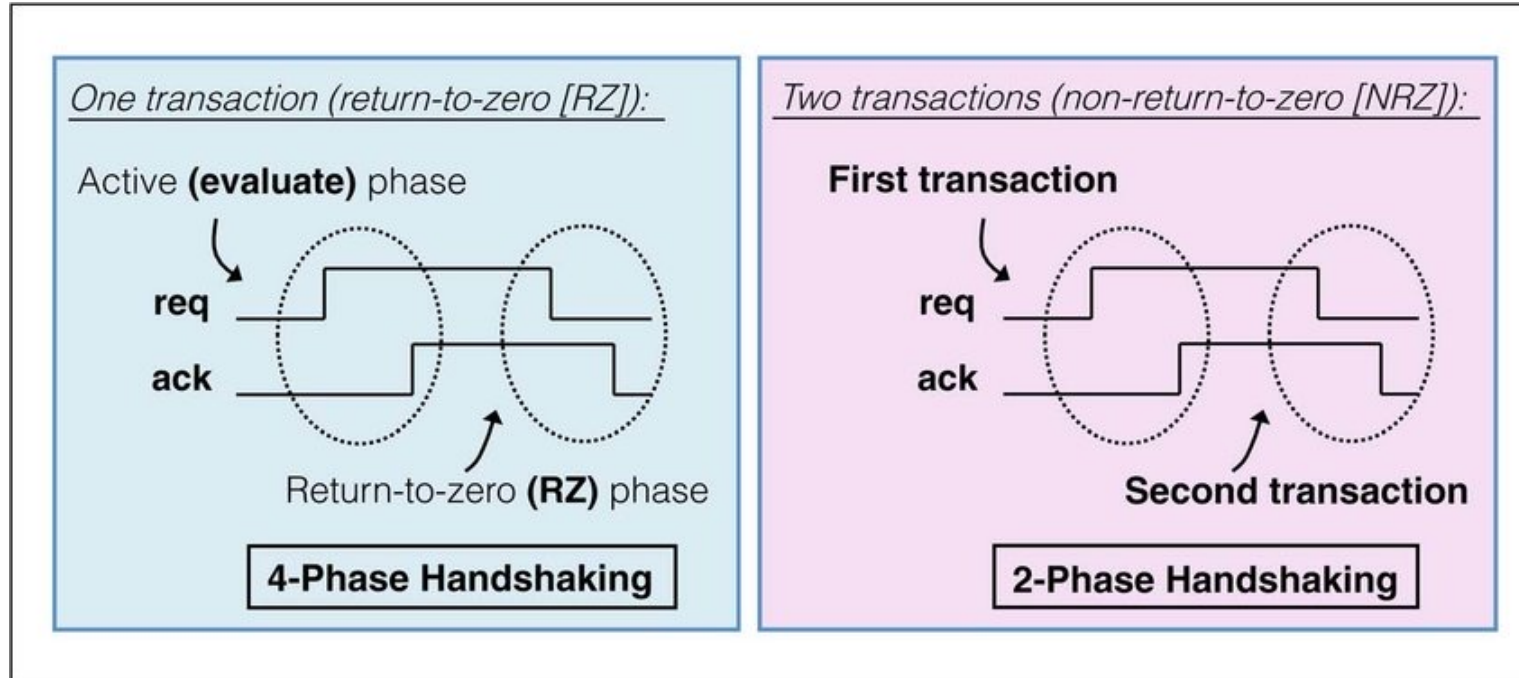

 - Hand-shaking is a good solution for multi-bit data to address the issue of synchronizer
- But, speed is limited → 2-phase version achieves better speed



Hand Shaking Implementation Details

 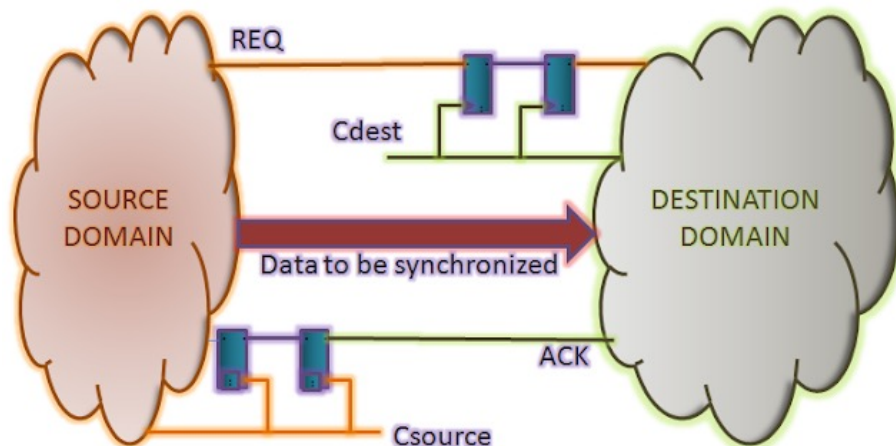

- Data should be prepared before REQ signal
- REQ signal at the receiver is synchronized with receiver clk → no setup/hold time issue
- If REQ is high at the receiver, it means the data is already valid
→ thus, capture the data & enable ACK signal
- ACK is synchronized at transmitter CLK → no setup/hold time issue
- Once ACK is high at transmitter, it means the data has been captured by receiver
→ thus, REQ is disabled and another data packet can be issued

FIFO (First-in First-out)



▪ FIFO at the async. interface

- Synchronizer is fast but for a single bit
- Hand shaking is for multi-bit but slow
- FIFO is most widely used solution as it is fast and multi-bit
- FIFO is also used within the same clk domain when in / out rates are different

Synchronous (Single-CLK) FIFO Implementation

■ FIFO with same clock domain

- Assume transmitter & receiver are at same clock domain
- But writing and reading are done at random timing
- When the FIFO depth is 2^D , equip $D+1$ bits of $rd_ptr[D:0]$ and $wr_ptr[D:0]$
- Whenever new value is written, $wr_ptr \leq wr_ptr + 1$
- Whenever new value is, read $rd_ptr \leq rd_ptr + 1$
- Note data does not move in the array, but only pointer increments
- wr_ptr and rd_ptr wrap around even after it reaches 2^D without resetting to zero
- Current output is given as a combinational logic, i.e., $assign\ out = array[rd_ptr]$
- if $wr_ptr == rd_ptr$, there is no contents, i.e., $empty \leq 1$, and receiver cannot read any more
- if “ $abs(wr_ptr - rd_ptr) == 2^D$ ”, the fifo is full, i.e., $full \leq 1$, and transmitter cannot send any more
- Above condition is equivalent to $(wr_ptr[D-1:0] == rd_ptr[D-1:0]) \ \&\& \ (wr_ptr[D] != rd_ptr[D])$




Verilog Example



■ FIFO with same clock domain

- Assume each data is 4 bit, and FIFO depth is 64
- Send data "data2.txt", which included 64 sequence through the FIFO
- Check the received data are same as the sent data with similar method in HW1
- Check rp_ptr (read pointer) and wr_ptr and the contents and output

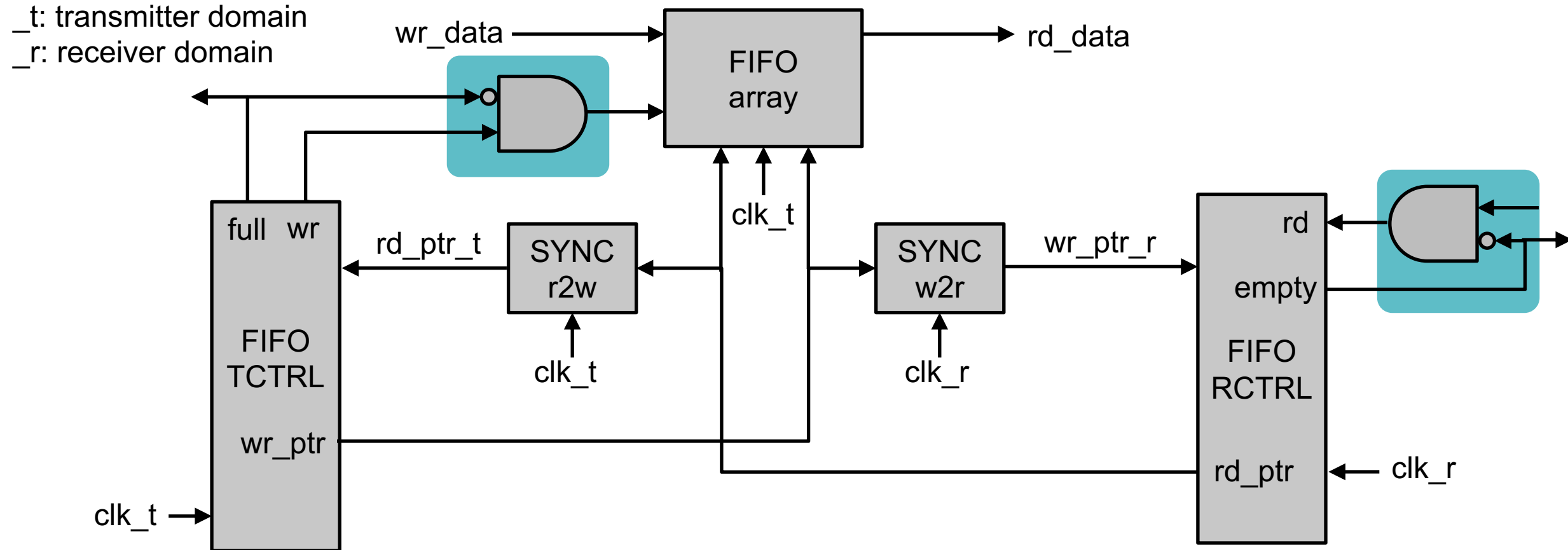Asynchronous (Dual-CLK) FIFO Implementation




- wr_ptr / rd_ptr are exchanged through synchronizer to produce full and empty signals
- wr_ptr is not incremented when $full = 1$ while rd_ptr is not incremented while $empty = 1$
- full and empty signal should be given to transmitter and receiver circuitry to inform wr / rd are not available


Issues in FIFO at Clock Domain Crossing

- Note multi-bit rd_ptr / wr_ptr cannot cross the async. interface
→ Gray code is required
- Relying on full / empty might not be the best practice considering system response time
→ It is safe to equip “almost full” and “almost empty” signals when *th* number before full or empty happens

Binary Code

 

Gray Code

 

Gray Code

Decimal Count	Binary Count	Gray Code Count
0	4'b0000	4'b0000
1	4'b0001	4'b0001
2	4'b0010	4'b0011
3	4'b0011	4'b0010
4	4'b0100	4'b0110
5	4'b0101	4'b0111
6	4'b0110	4'b0101
7	4'b0111	4'b0100
8	4'b1000	4'b1100
9	4'b1001	4'b1101
10	4'b1010	4'b1111
11	4'b1011	4'b1110
12	4'b1100	4'b1010
13	4'b1101	4'b1011
14	4'b1110	4'b1001
15	4'b1111	4'b1000

```

assign gray[0] = binary[1] ^ binary[0];
assign gray[1] = binary[2] ^ binary[1];
assign gray[2] = binary[3] ^ binary[2];
assign gray[3] = binary[3];

```


```

assign binary[0] = gray[3] ^ gray[2] ^ gray[1] ^ gray[0];
assign binary[1] = gray[3] ^ gray[2] ^ gray[1];
assign binary[2] = gray[3] ^ gray[2];
assign binary[3] = gray[3];

```

- Gray code toggles only one bit at a time
- Safely transfer the data through the synchronizer
- Gray code exists only for 2^N total counts (code is N-bit)
- Thus, FIFO depth should be 2^N

Gray Counter

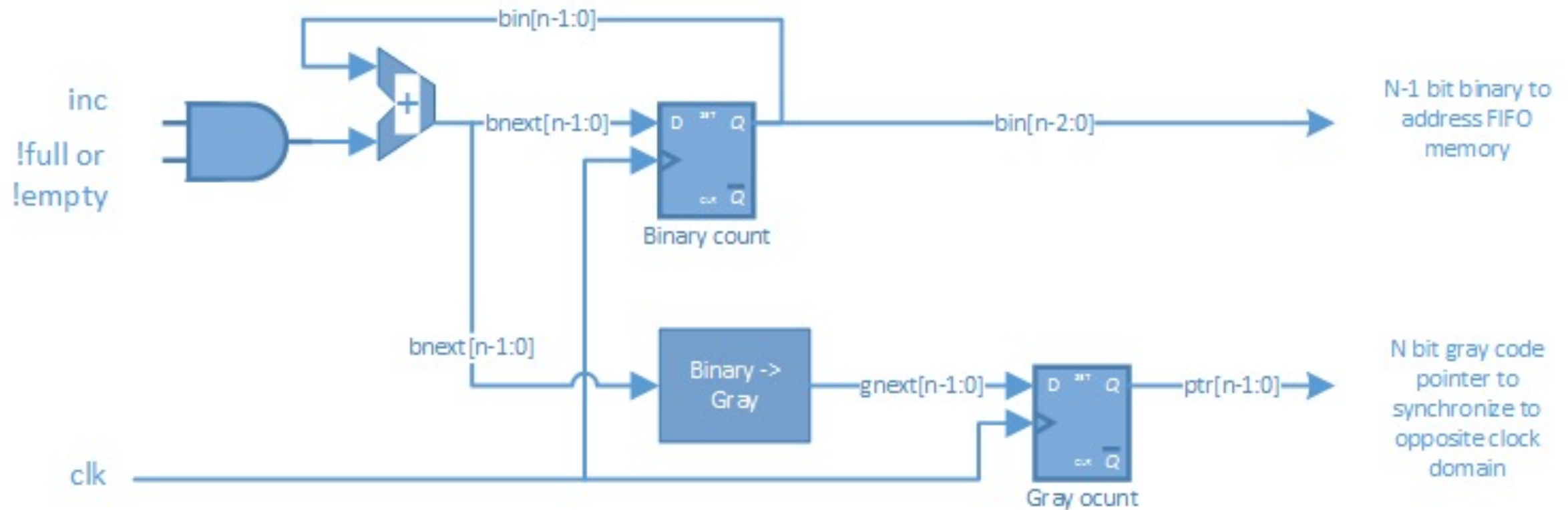

- Binary-> Gray converter is embedded in the counter

FIFO Depth Calculation

$$\text{fifo_depth} = B - B * \text{freq}_{\text{rd}} / \text{freq}_{\text{wr}}$$

here, B : data packet size, freq_{wr} : data writing rate, freq_{rd} : data reading rate


Proof

- Time to fill the B data with $\text{freq}_{\text{wr}} = B / \text{freq}_{\text{wr}}$
- Number of data read meanwhile = $\text{freq}_{\text{rd}} * (B / \text{freq}_{\text{wr}})$
- Thus, the data not read should be buffered
- Thus, $B - B * \text{freq}_{\text{rd}} / \text{freq}_{\text{wr}}$

 Example

- freq_{wr} : 30MHz
- freq_{rd} : 20MHz
- Writing Burst Size = 10
- Then, buffer size = $10 - 10 (20/30)$
 $= 3.33$
 Thus, 4


HW1: Bi-direction Async. Interface with Hand-shaking



■ Asynchronous interface verilog design

- Build bi-directional async. interface with verilog, i.e., both sides can be either receiver / transmitter
- Note new request can start when there is no on-going transaction
- e.g., you need to build a simple state machine to issue req and ack signals accordingly
- You also need to equip the synchronizer for the req / ack for both directions.
- Frequency is 1 GHz & 1.5 GHz
- Your data is “data.txt” from HW
- Build test bench to store initial “data.txt” in a big register inside test bench (This is not a part of your DUT, but just for convenience.)
- Then, send from left to right all the contents in “data.txt” file. Then, send all the contents back to from right to left
- Compare your received data at the left with the initial data in a big register in the testbench.

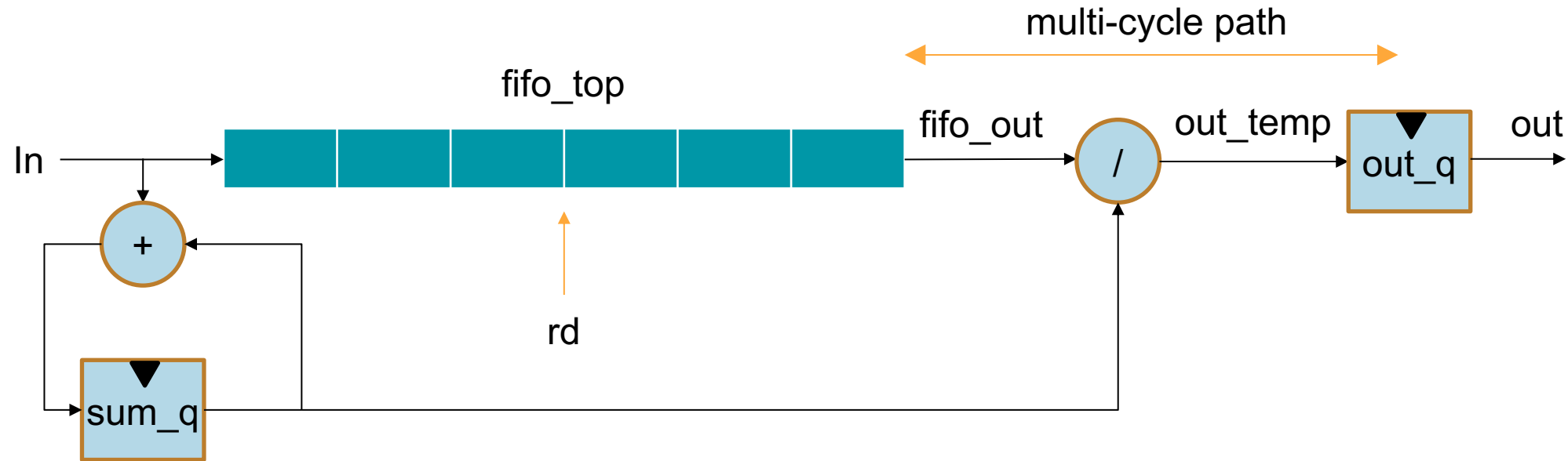HW2: Normalization (FIFO + Multi-cycle Path)



■ Normalization

- Assume your inputs are unsigned numbers
- While writing you get the sum of the elements (`b_data.txt`)
- $(\text{fifo_out} / \text{sum_q}) * 256$ is given to `out_q` register
- Design your normalizer by modifying the given Verilog code
- Synthesize with 1GHz + 0.2ns IO delay + Typ corner
- Apply multi-cycle path until you meet the 0 WNS from the synthesized result

Hint) remove all the inherited parameters
e.g., `#(.bw(bw))`