

# **ECE260B Winter 22**

## **Memory**

**Prof. Mingu Kang**

**UCSD Computer Engineering**

# Midterm Statistics

Ⓜ Average Score

**71%**

↗ High Score

**99%**

↘ Low Score




Ⓢ Standard Deviation

**10.25**

🕒 Average Time

**01:09:57**

• • •

 


**Great job !**

# Rebuttal Policy

- Score will be given by the end of tomorrow (Feb 25)
- Answer will be given, and simple solution will be given for calculation questions
- Submit your rebuttal through the comment in Canvas or email by 1PM Feb 28 (Mon), **No exception whether you see this message or not. No rebuttal accepted after deadline**
- No question allowed related to midterm problem before Feb 28<sup>th</sup> 1 PM
- Only one rebuttal opportunity is given, thus describe your logic as clear as possible
- Simply describing your assumption in Q1 does not guarantee a credit
- No in-person verbal rebuttal allowed to be synchronous
 
# Processor Area Becoming Memory Dominated

Intel® Core™ i7-3960X Processor Die Detail



- **On chip SRAM contains 50-90% of total transistor count**
  - Xeon: 48M/110M
  - Itanium 2: 144M/220M
- **SRAM is a major source of chip static power dissipation**
  - Dominant in ultra-low power applications
  - Substantial fraction in others


# Energy in Computation vs. Memory

Integer	
Add	
8 bit	0.03pJ
32 bit	0.1pJ
Mult	
8 bit	0.2pJ
32 bit	3 pJ


FP	
FAdd	
16 bit	0.4pJ
32 bit	0.9pJ
FMult	
16 bit	1pJ
32 bit	4pJ

Memory	
Cache	(64bit)
8KB	10pJ
32KB	20pJ
1MB	100pJ
DRAM	1.3-2.6nJ

- 8 cores
- L1/reg/TLB
- L2
- L3

 


# SRAM Architecture

 

- Total  $2^{(m+n)}$  bits
- Word size =  $2^m$  bits
- Column mux ratio =  $2^k:1$
- Sense amp / Write driver shared every  $2^k$  columns
- $2^k-1$  columns are discharged unnecessarily

# SRAM Operations

 


## Traditional 6-Transistor (6T) SRAM cell

# Three tasks of a cell

- Hold (data retention)
  - WL=0; BLs=X
- Write
  - WL=1; BLs driven with new data
- Read
  - WL=1; BLs precharged and left floating

# SRAM Cell Metrics

 

Traditional 6-Transistor (6T)  
SRAM cell


## Key functionality metrics

- Hold (Data retention)
  - Static Noise Margin (SNM)
  - Data retention voltage (DRV)
- Read
  - Static Noise Margin (SNM)
- Write
  - Write Margin





# Retention Mode


 


Source: Cypress/ICE, "Memory 1997"

22460

- Supply voltage is lowered during retention mode to minimize leakage
- SNM is further reduced
- $t_{CDR}$ : time to switch to retention mode
- $t_R$ : time to recover from retention mode
- Note above diagram assumes the retention mode begins with CE enabling, but sometimes there is extra pin (e.g., RET pin)




# Read static Noise Margin (RSNM)

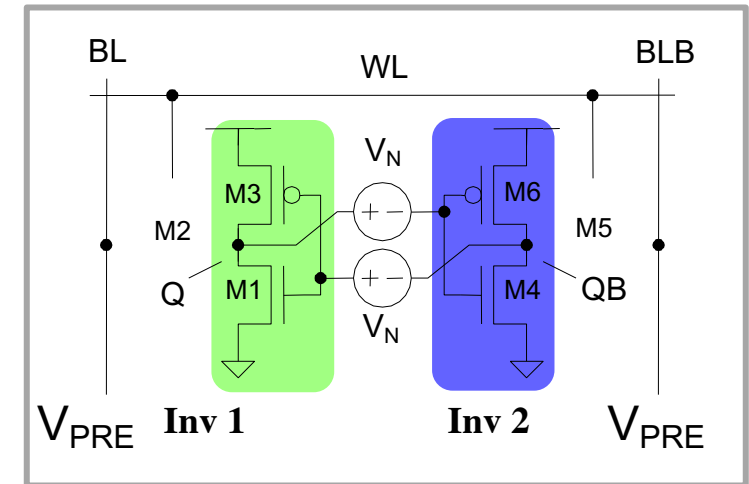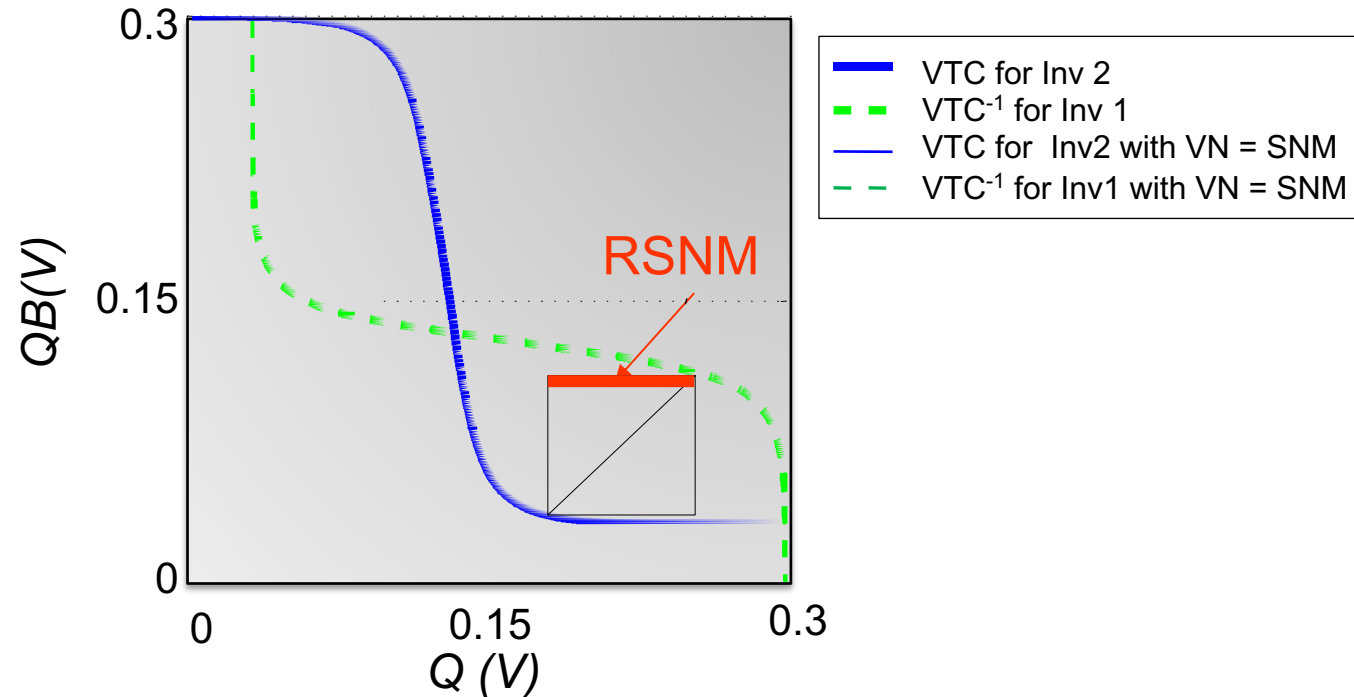

- $V_{\text{PRE}}$  is floating voltage, but assume that it is forced for the worst-case consideration


- RSNM: similar to SNR, but set the BL & BLB voltages to be  $V_{\text{PRE}}$  to emulate the read operation
- $I_{M4} > I_{M5}$ , otherwise the data will be flipped (lost)

# Write Margin

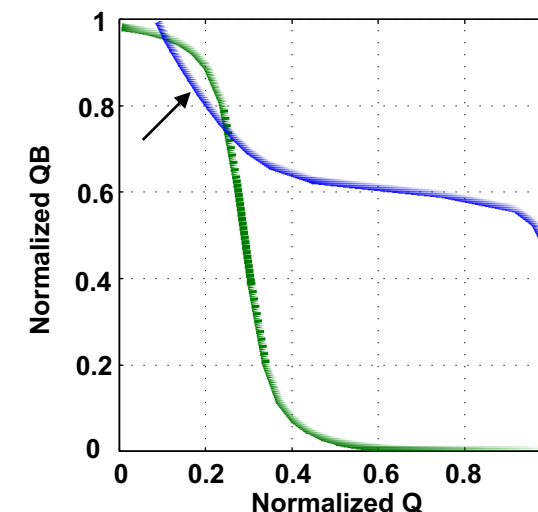  

- Data 0 should be written to QB by flipping the current data 1
- Note, data 1 cannot be written as  $I_{M4} > I_{M5}$
- $I_{M5} > I_{M6}$ , otherwise the data 0 cannot be written
- Thus,  $I_{M4} > I_{M5} > I_{M6}$


# 8-T SRAM Bitcell

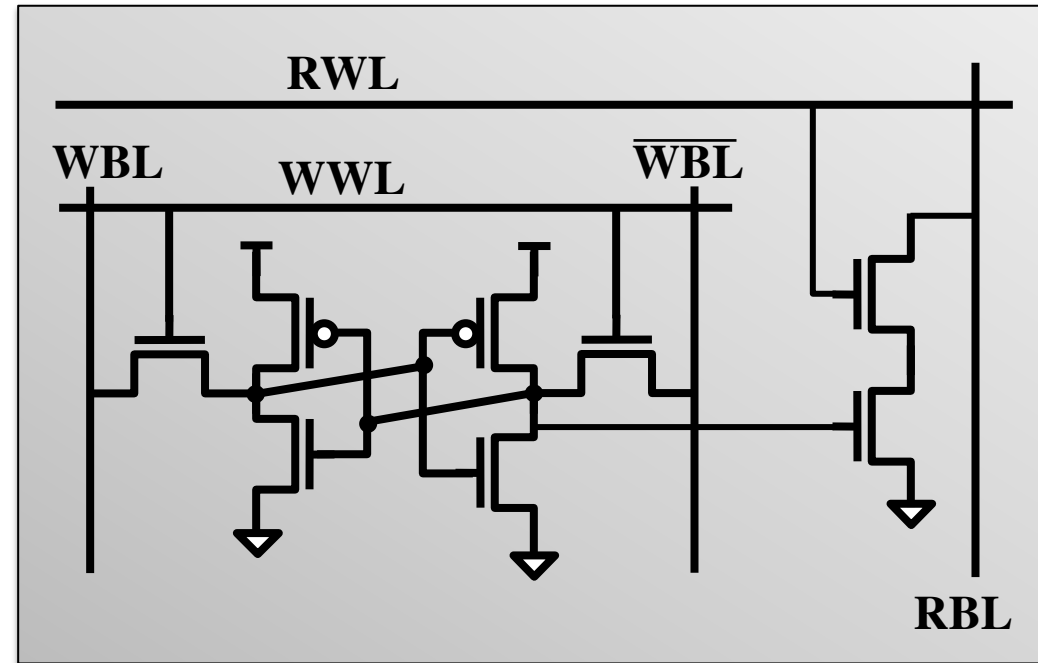

8T SRAM cell


- Key tradeoff is with functional robustness (e.g. Remove read SNM) vs. 30% area overhead
- Dual port support (1R / 1W port) – suitable for register file
- Allows lower  $V_{DD}$

# Dual-port SRAM (Register File)

 

- Another type of dual-port SRAM
- Both ports (A and B) can be used either read and write functionality


# Leakage Currents

 

- Leakage Power dominates while the memory holds data (Stand-by mode)
- Supply voltage is reduced to minimize the leakage current (so called, sleep mode or retention mode or stand-by mode) -> but, causes lower SNR

# Memory Compiler-based Single-port SRAM (SPSRAM)


## Logic Symbol

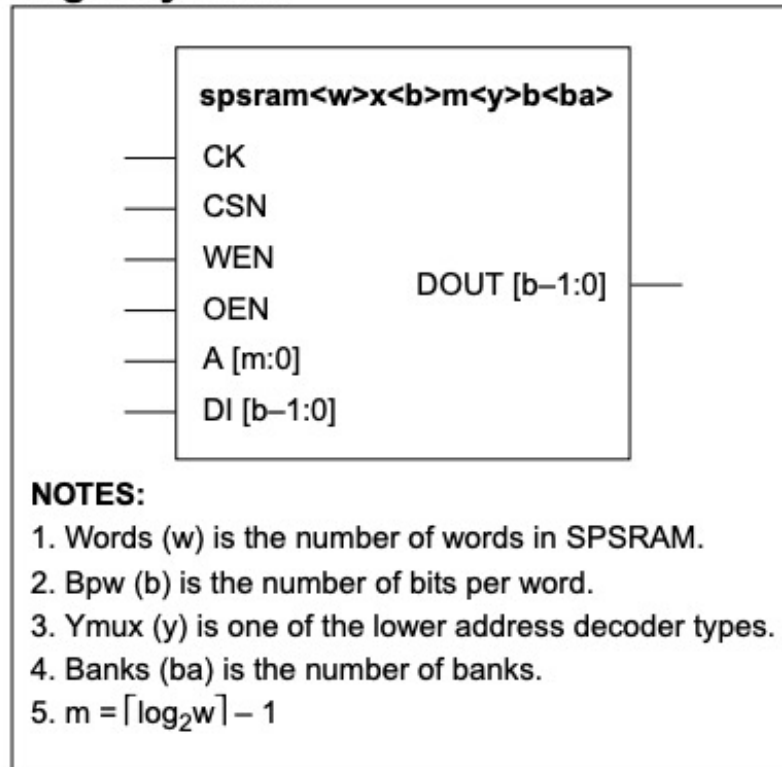


- CSN (or CEN): chip select negative
- OEN: output enable negative  
@OEN = 1, DOUT is tri-state
- A: address
- DI (or D): input data
- DOUT (or Q): output data
- RETN: retention mode enable



# Read and Write Timing Diagram

 


(a) Read operation timing

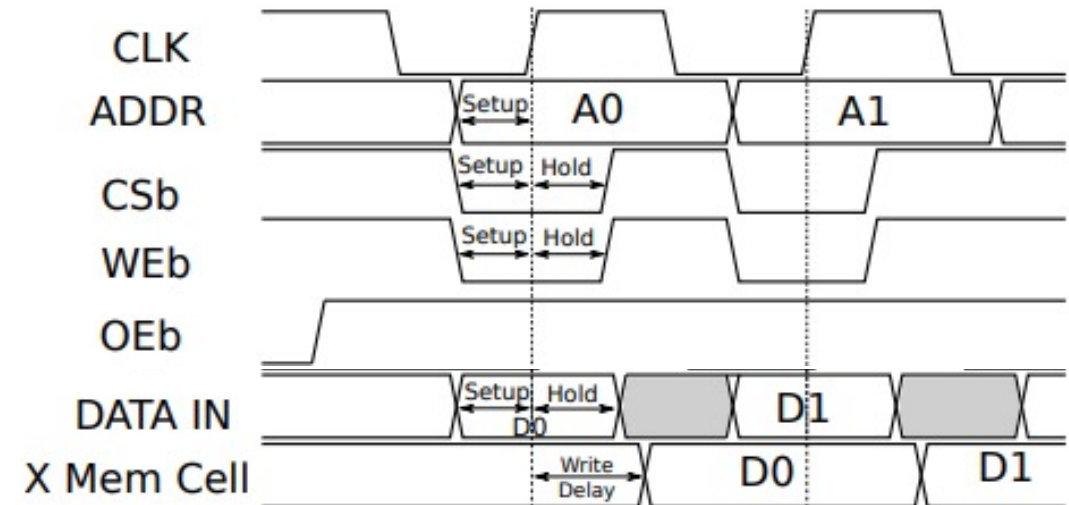

(b) Write operation timing

# Multi-bank SRAM Layout

 

# Example of Memory Compiler Options

Parameters		YMUX = 2	YMUX = 4	YMUX = 8	YMUX = 16	YMUX = 32
Words (w)	Min	4	8	16	32	64
	Max	512	1024	2048	4096	8192
	Step	2	4	8	16	32
Bpw (b)	ba = 1	Min	1	1	1	1
		Max	128	64	32	16
		Step	1	1	1	1
	ba = 2	Min	2	2	2	2
		Max	256	128	64	32
		Step	1	1	1	1

- Bpw: bit width per word
- YMUX = column mux
- ba: # of banks

# Timing and Power Specs


## 1) Timing Characteristics [Unit: ns]

Timing Type	Timing Equation
	<b>Y = 2</b>
cycle_time	$(5.8213e-03 * W + 1.1171e-02 * B / BA + 9.6628e-01 * 0.02 * SL + 3.7318) * 1.08$
minckh	$(1.9096e-03 * W + 2.4791e-03 * B / BA + 1.2200 * 0.02 * SL + 2.1295)$
minckl	$(2.1603e-03 * W + 3.5437e-03 * B / BA + 1.7035 + 2.8208e-07 * W * B / BA)$
tacc	$(2.8038e-03 * W + 5.8650e-03 * B / BA + 1.7115e-01 * S + 4.9717e-01 * 0.02 * SL + 2.3023)$
	<b>Y = 4</b>
cycle_time	$(2.9106e-03 * W + 2.2342e-02 * B / BA + 9.6628e-01 * 0.02 * SL + 3.7318) * 1.08$
minckh	$(9.5482e-04 * W + 4.9583e-03 * B / BA + 1.2200 * 0.02 * SL + 2.1295)$
minckl	$(1.0801e-03 * W + 7.0874e-03 * B / BA + 1.7035 + 2.8207e-07 * W * B / BA)$
tacc	$(1.4019e-03 * W + 1.1730e-02 * B / BA + 1.7115e-01 * S + 4.9717e-01 * 0.02 * SL + 2.3023)$
	<b>Y = 8</b>
cycle_time	$(1.4553e-03 * W + 4.4684e-02 * B / BA + 9.6628e-01 * 0.02 * SL + 3.7318) * 1.08$
minckh	$(4.7741e-04 * W + 9.9166e-03 * B / BA + 1.2200 * 0.02 * SL + 2.1295)$
minckl	$(5.4009e-04 * W + 1.4174e-02 * B / BA + 1.7035 + 2.8208e-07 * W * B / BA)$
tacc	$(7.0097e-04 * W + 2.3460e-02 * B / BA + 1.7115e-01 * S + 4.9717e-01 * 0.02 * SL + 2.3023)$
	<b>Y = 16</b>
cycle_time	$(7.2766e-04 * W + 8.9369e-02 * B / BA + 9.6628e-01 * 0.02 * SL + 3.7318) * 1.08$
minckh	$(2.2870e-04 * W + 1.0822e-02 * B / BA + 1.2200 * 0.02 * SL + 2.1295)$

## 2) Power Characteristics [Unit: $\mu$ W]

Power Type	Power Equation
	<b>Y = 2</b>
power_ck	$(1.7046e-01 * W + 8.7926e-01 * B + 1.2869 + 7.9009e-04 * W * B) * VDD^2 * F$
power_csn	$(4.6346e-03 * W + 1.3484e-01 * B + 5.8215e-01 - 9.0563e-05 * W * B) * VDD^2 * F$
	<b>Y = 4</b>
power_ck	$(8.5232e-02 * W + 1.7585 * B + 1.2869 + 7.9009e-04 * W * B) * VDD^2 * F$
power_csn	$(2.3173e-03 * W + 2.6969e-01 * B + 5.8215e-01 - 9.0563e-05 * W * B) * VDD^2 * F$
	<b>Y = 8</b>
power_ck	$(4.1803e-02 * W + 3.3360 * B + 3.3968e-01 + 6.4193e-04 * W * B) * VDD^2 * F$
power_csn	$(1.1586e-03 * W + 5.3939e-01 * B + 5.8215e-01 - 9.0563e-05 * W * B) * VDD^2 * F$
	<b>Y = 16</b>
power_ck	$(1.8749e-02 * W + 5.2054 * B + 3.5471 + 8.7095e-04 * W * B) * VDD^2 * F$
power_csn	$(5.7933e-04 * W + 1.0787 * B + 5.8215e-01 - 9.0563e-05 * W * B) * VDD^2 * F$
	<b>Y = 32</b>
power_ck	$(9.0824e-03 * W + 9.4829 * B + 4.6843 + 7.9026e-04 * W * B) * VDD^2 * F$
power_csn	$(2.8966e-04 * W + 2.1575 * B + 5.8215e-01 - 9.0563e-05 * W * B) * VDD^2 * F$
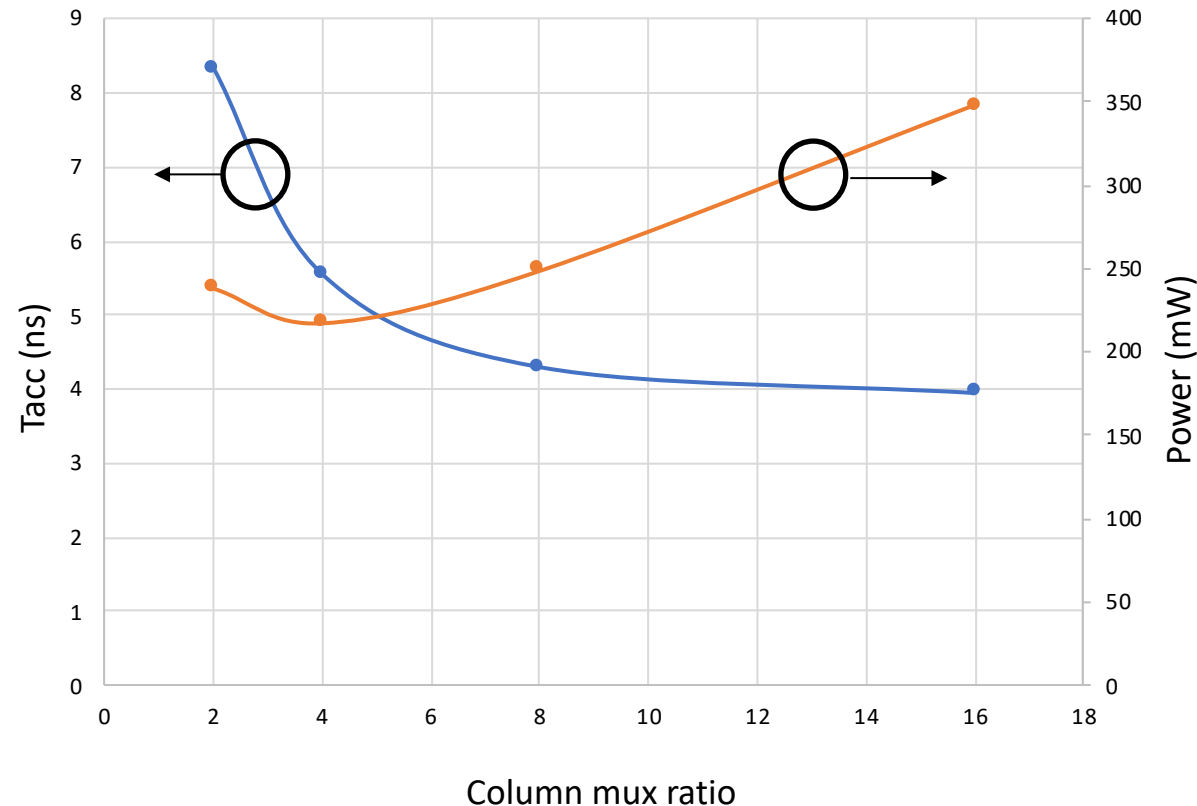
# Access Time and Power w.r.t. Column Mux Ratio




## Setting

- number of words = 2048
- bit per word = 16 bits
- $V_{DD} = 1V$
- Freq = 1 GHz


- Higher column mux leads to fast read operation, but higher power consumption
 
# Power & Speed Trade-off w.r.t. Column Mux Ratio



Column mux = 2:1


 
- long BLs: slow operation
- But, only 2 columns read at a time per 1 bit read



Column mux = 8:1


- Short BLs: fast operation
- But, 8 columns read at a time per 1 bit read
- Large energy consumption
 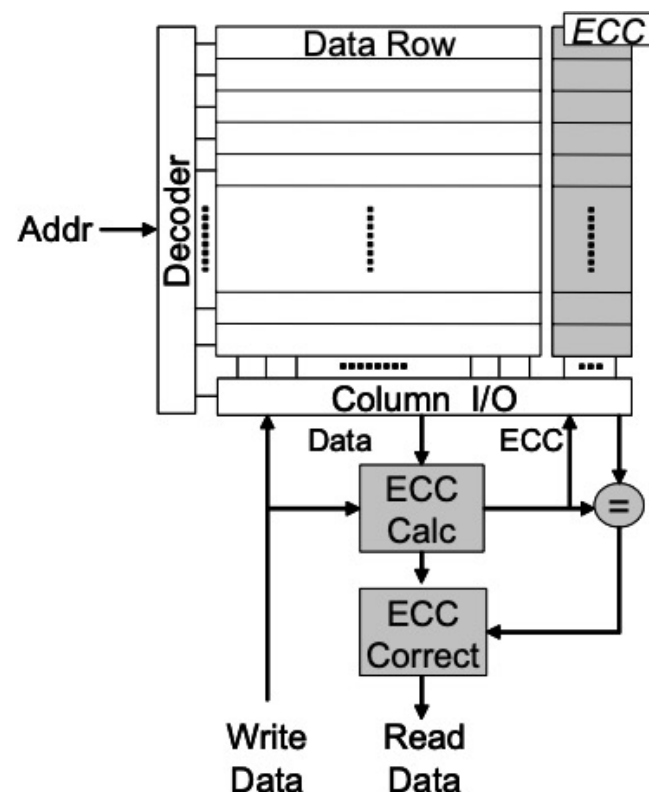
# Error Correcting Code Constraints w.r.t Column Mux




- Multi-bit failure per word is more difficult to correct by error correcting code
- Thus, bits in a word are interleaved to be spread (far each other spatially)
- The interleaving avoids multi-bit failure by alpha particles
- Higher tolerance with higher bit interleaving (column mux) ratio at the expense of power increase

# Memory Double Buffering

 


Writing

 


Reading

Without double buffering

 - Processor needs to wait whiling writing



read & write during period1

 

read & write during period2

With double buffering


- Processor can be operated all the time
- Two independent memory banks are required



# Synchronous vs. Asynchronous SRAM


- Synchronous SRAM
  - Operations are synched with clock,
  - i.e., controls, address, data are accepted at the rising (of falling) edge of clock
- Asynchronous SRAM
  - $WEN = 1$ , whenever address changes, new data read
  - $WEN = 0$ , whenever the  $WEN$  is disabled, new data is written

# Memory Layout Considerations

 

- Memory layout is (of course) square box
- If the same capacity of memory is decomposed into 2 banks, the area becomes more than twice
- It is preferred the data pitch matches between memory vs. processor
- Memory compiler-generated layout uses low metals (e.g., up to M5), so you can route over memory

# [Example] Memory Write and Read

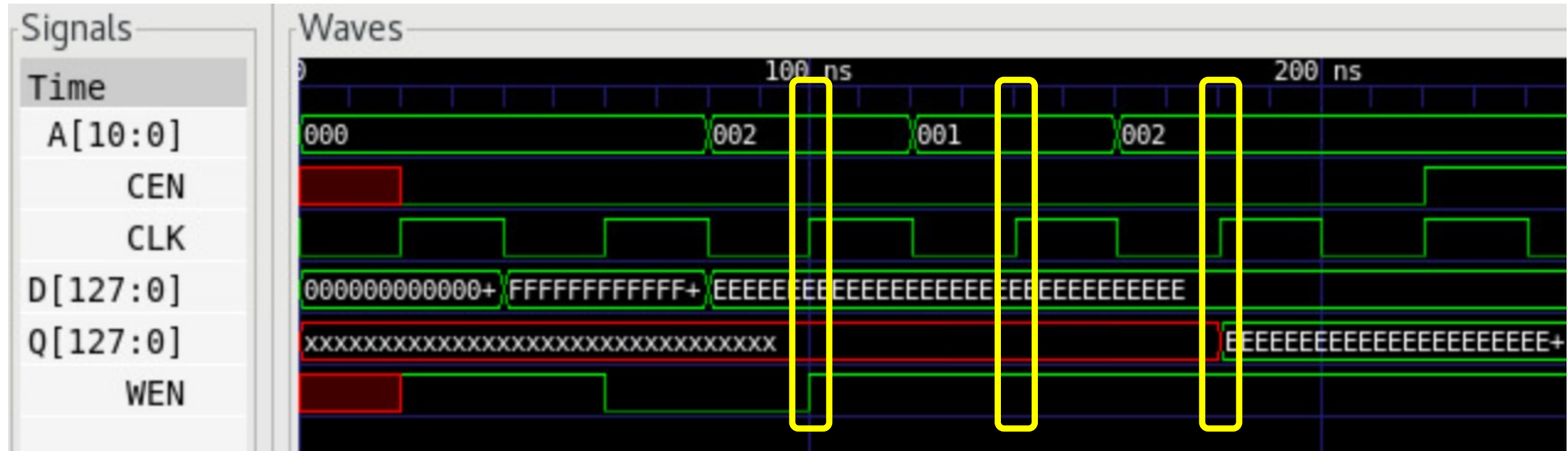

1. “WEN=0 & ADD = 002 & D = EEEEE..” are received by SRAM
2. “WEN=1 & ADD = 001” are received by SRAM
3. “WEN=1 & ADD = 002” are received by SRAM

From tb, it is good to apply new input at CLK = 0, or pass through register

# [Example] Memory Write and Read


- Write 'data.txt' file contents into the memory at the address of 0 – 15.
- Then, read the memory from the address of  $A = 0 - 15$ .
- Compare the read data is the same as expected in the 'data.txt' file in the testbench

# [HW2] Memory Write and Read with Double Buffering


- You need to write 32 contents and read subsequently
- But, your memory has a limited space with 16 words.
- You have two SRAMs, EVEN and ODD memories.
- Write  $0^{\text{th}} - 15^{\text{th}}$  contents into the EVEN memory at the address of  $0 - 15$ .
- Then, read the memory from the address of  $A = 0 - 15$  from EVEN memory while writing the  $16^{\text{th}} - 31^{\text{th}}$  contents into ODD memory simultaneously.
- Finally, read the  $16^{\text{th}} - 31^{\text{th}}$  contents from ODD memory.

# Project Description


# 2D Systolic-based Architecture

 

IBM Rapid

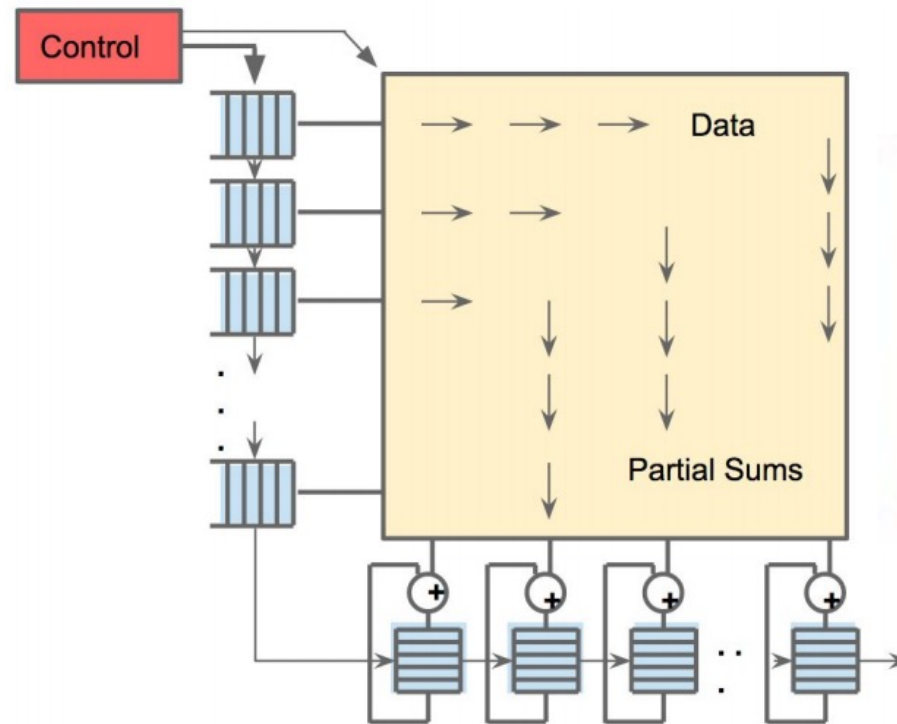

Google TPU

 


Intel Nervana

J.Oh, "A 3.0 TFLOPS 0.62V Scalable Processor Core for High Compute Utilization AI Training and Inference"


<https://arxiv.org/pdf/1704.04760.pdf>

<https://fuse.wikichip.org/news/3270/intel-axes-nervana-just-two-months-after-launch/>
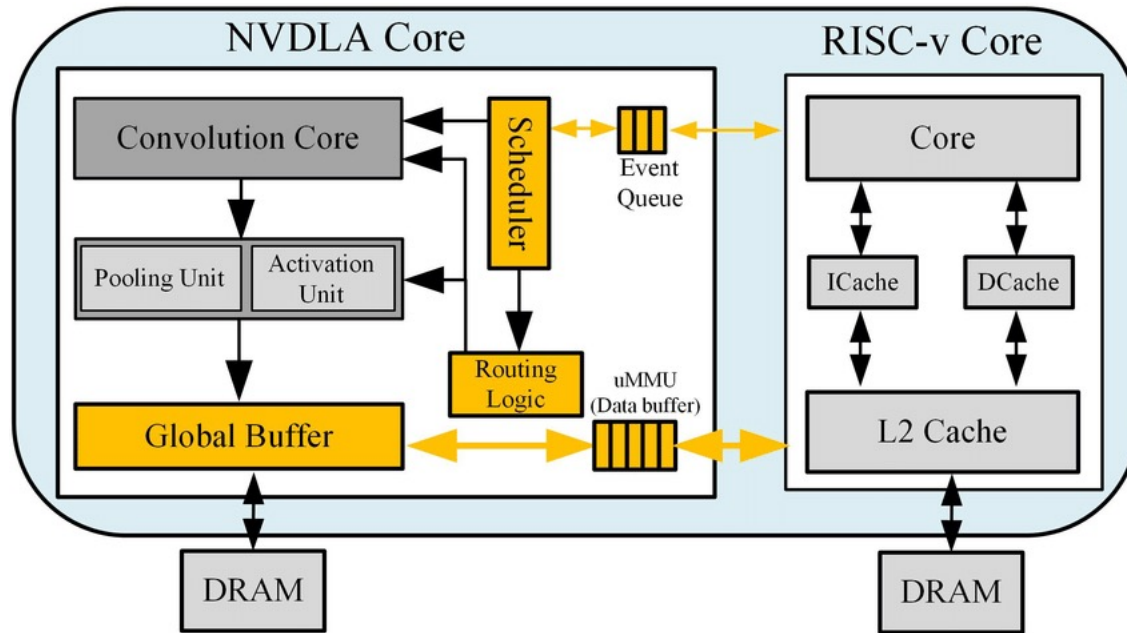
# 1-D Vector Processor based Architecture




**NVIDIA NVDLA**

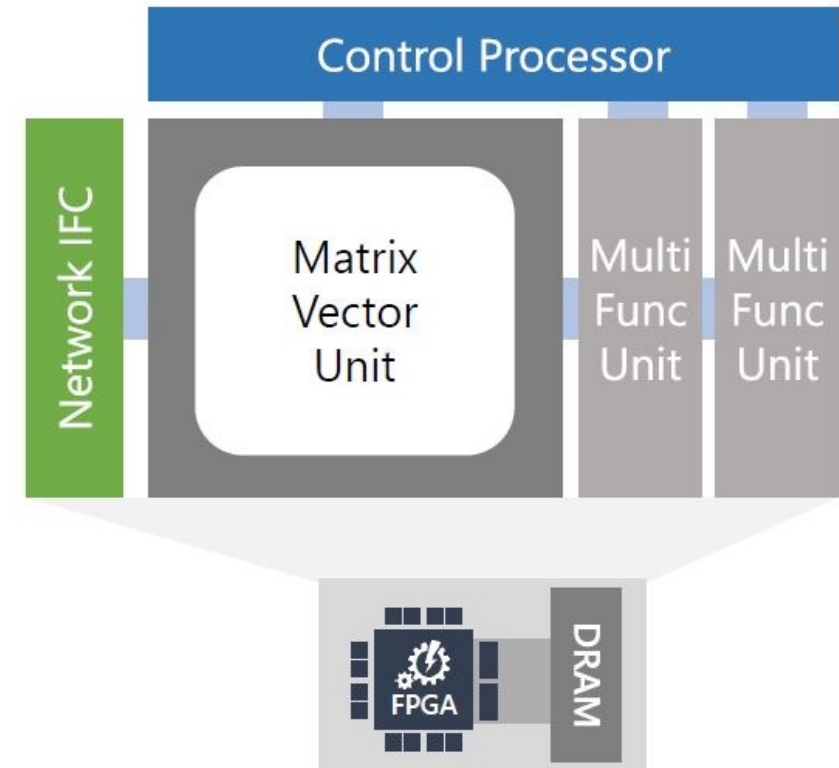


**Microsoft Brainwave**



# Architecture

 


1-D vector processor architecture

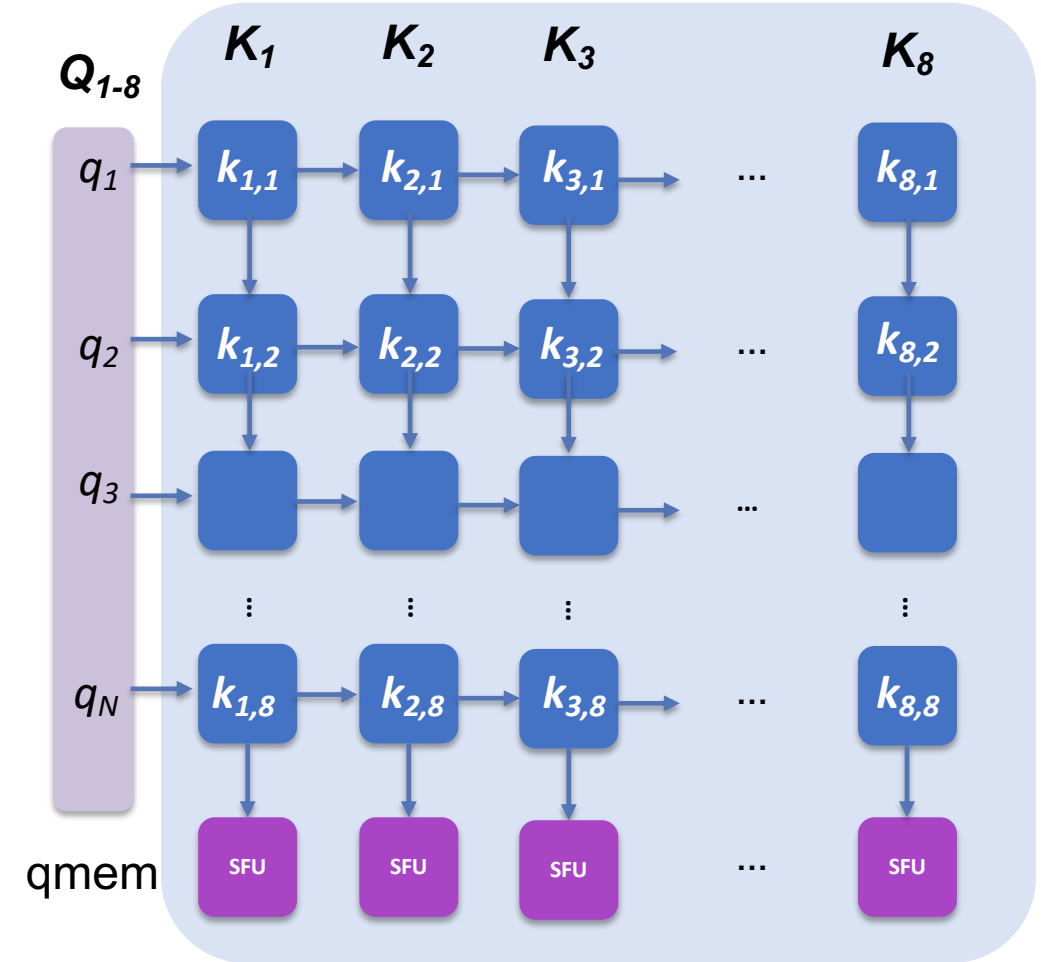


2D-systolic array architecture
 
# Front-end Computation in Transformer Model for Natural Language Processing




Facebook bAbi QA task processing


# Architecture

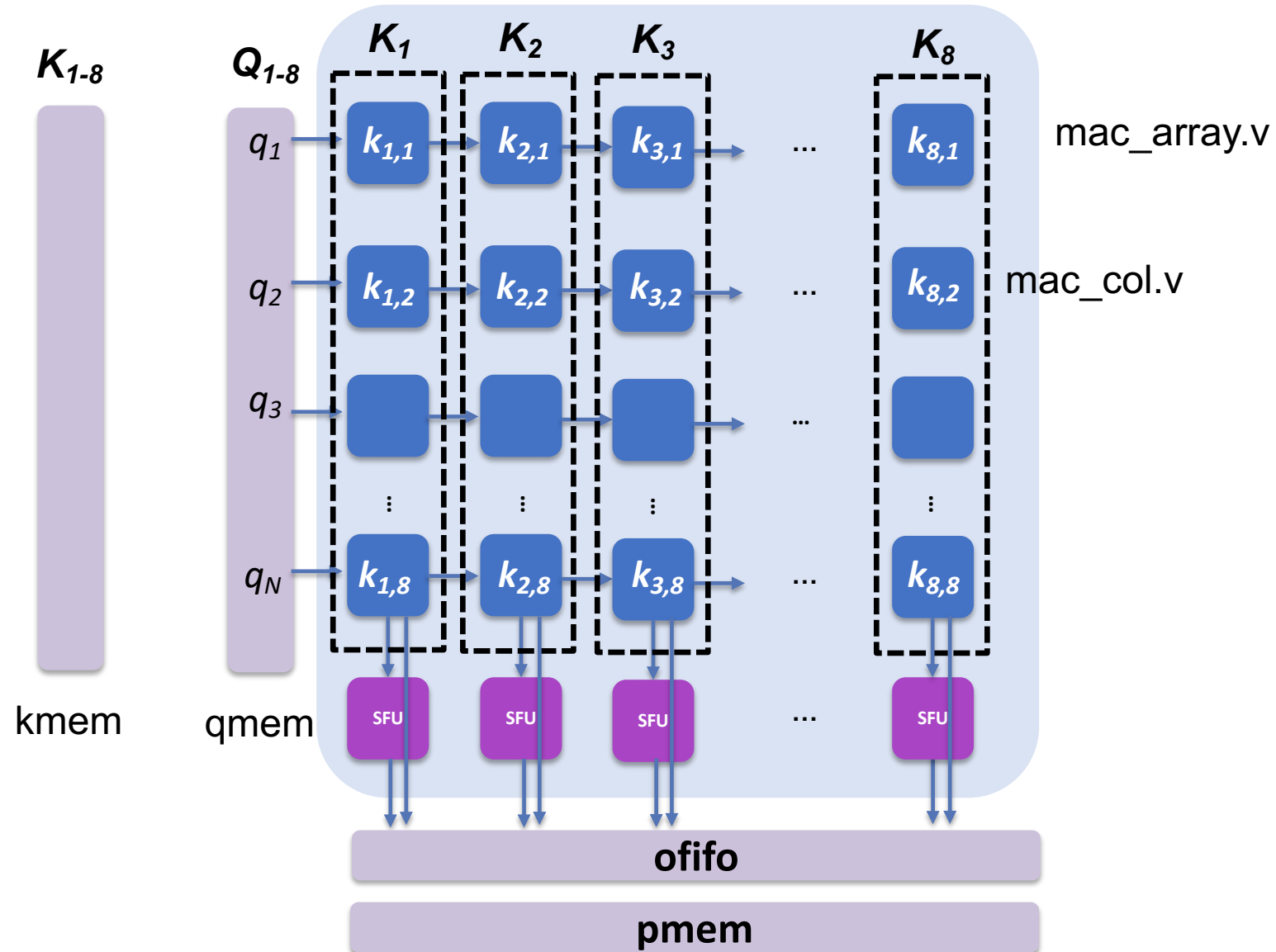


# Computation

 


# Computation

 

# Computation

 

# Computation


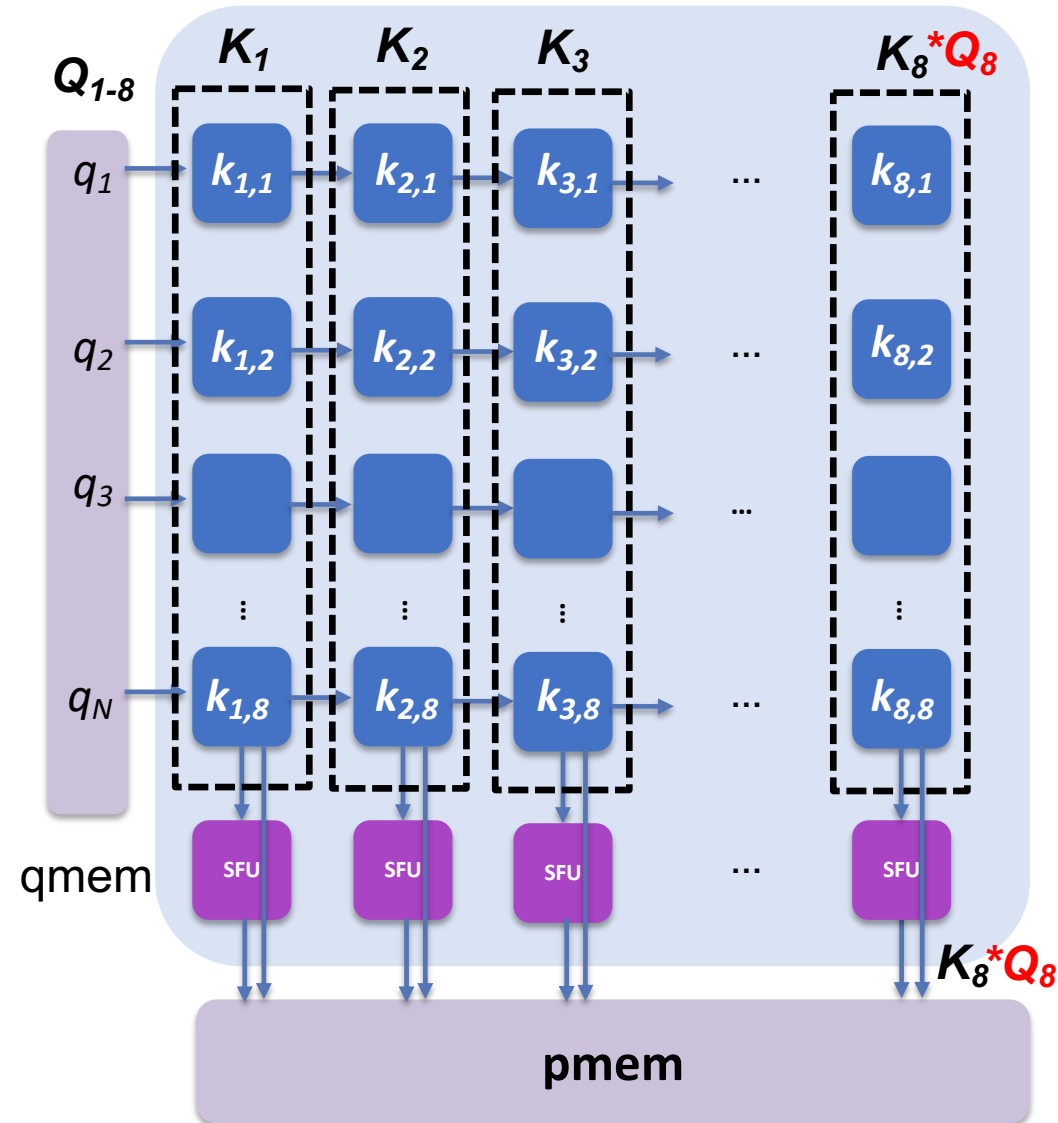


# Processing Stage

- Stage1: memory write stage
  - qmem & kmem: fill both memory with “qdata.txt” and “kdata.txt”
- Stage2: k-data loading stage
  - move the data from kmem to process’s local register
- Stage3: execute
  - move the data from qmem to input of the processor



# More Detail

 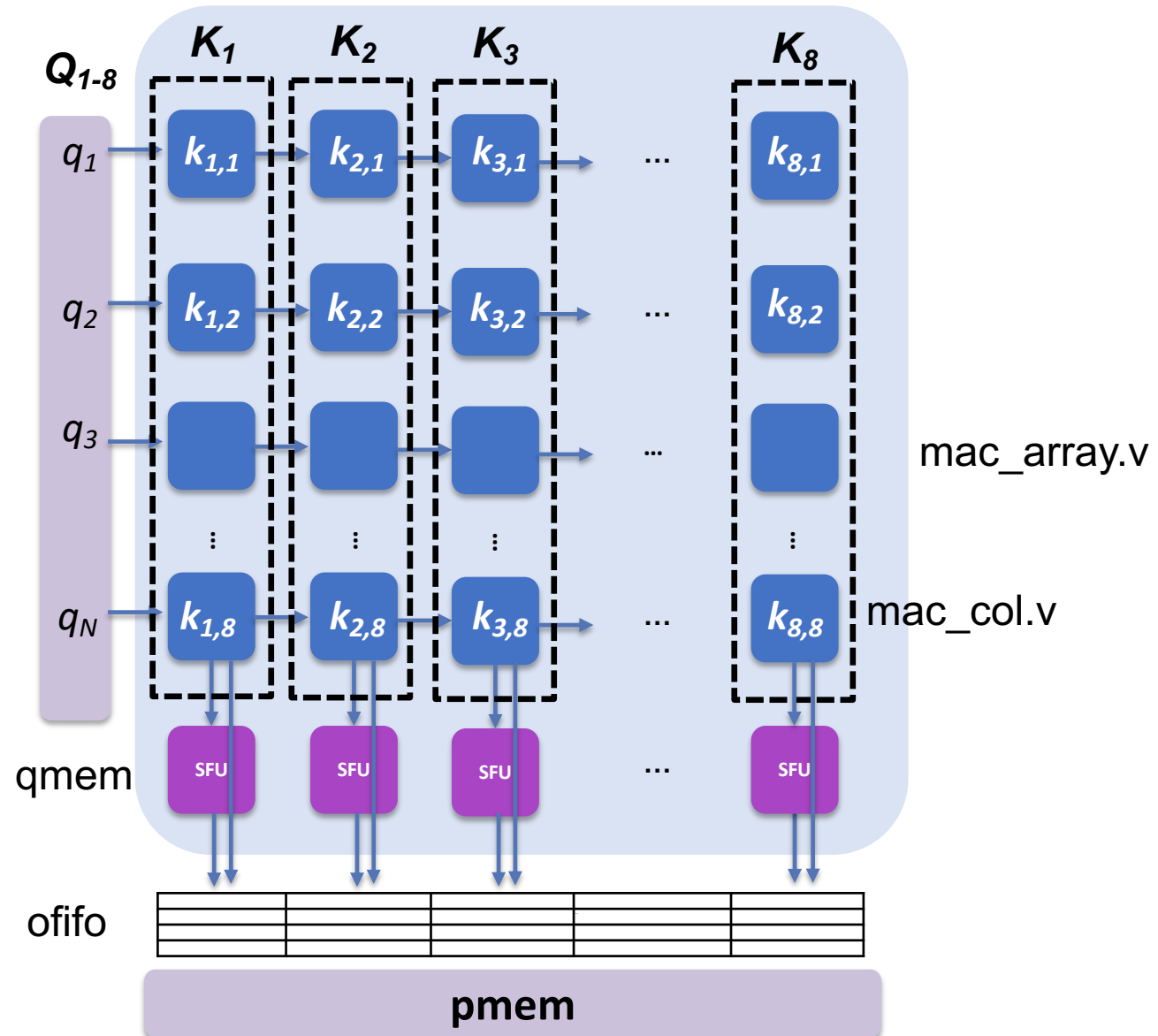

# OFIFO Operation

WR = 1



Black	White	White	White	White
White	White	White	White	White
White	White	White	White	White
White	White	White	White	White

cyc = 1

WR = 1 WR = 1 WR = 1



Black	Black	Black	White	White
Black	Black	White	White	White
Black	White	White	White	White
White	White	White	White	White

cyc = 3

WR = 1 WR = 1



Black	Black	White	White	White
Black	White	White	White	White
White	White	White	White	White
White	White	White	White	White

cyc = 2

WR = 1 WR = 1 WR = 1 WR = 1 WR = 1


ready to  
be read

Black	Black	Black	...	Black
Black	Black	Black	...	Black
Black	Black	White	White	White
Black	White	White	White	White


pmem

cyc = 8

# Normalization

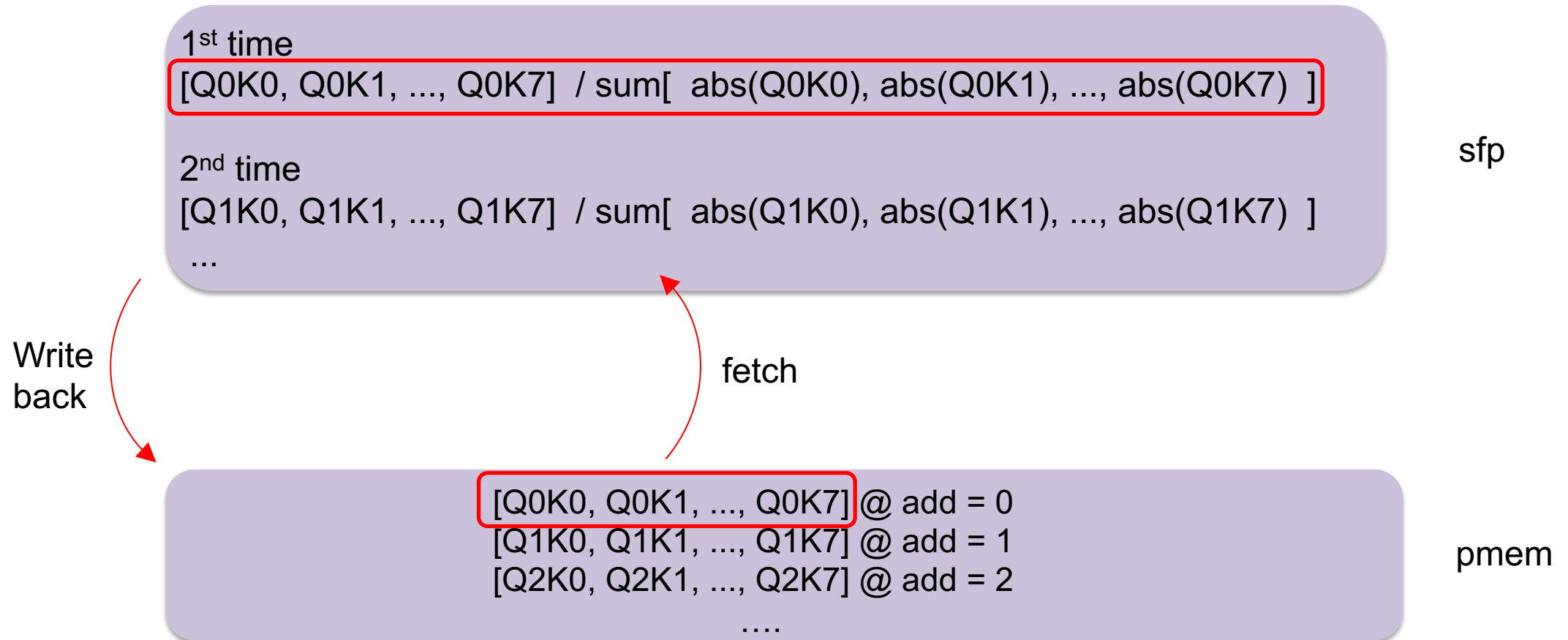

# Extension for Dual Core

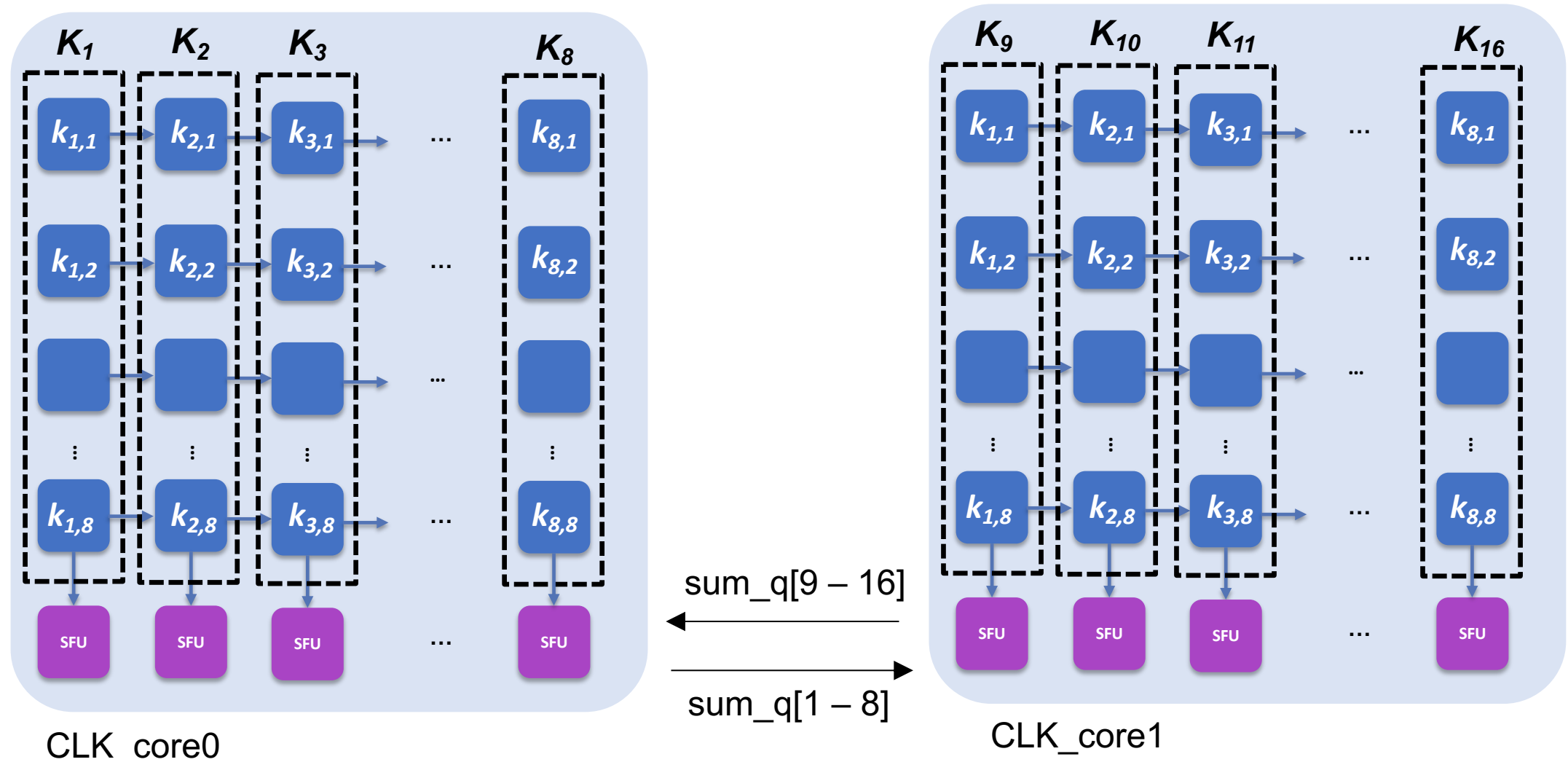

Normalize by “ $\text{sum}( \text{abs}(Q0K0), \text{abs}(Q0K1), \dots, \text{abs}(Q0K7) )$  from core0  
 $+ \text{sum}( \text{abs}(Q0K8), \text{abs}(Q0K9), \dots, \text{abs}(Q0K15) )$  from core1”

# Optimization

- Optimize the implementation to maximize the frequency and minimize power
  - However, the project is not a spec competition
- Apply techniques you have learned from this course
- Potential optimization (does not mean you need to do everything below)
  - Pipeline, multi-cycle path, memory double-buffering, clock gating, loop unrolling, more # of cores, any other creative idea
  - Async interface handling (synchronizer, hand shaking, ....)
  - Maximize parallelism between processing stages
  - Design your own controller
  - better verification (with random input)
  - Minimize WNS and DRC errors

# How to prove ?

- Prove the efficacy of your idea (why ? how ? how much ?)
  - measure power and check functionality with VCD  
(SDF is not required, but it will be plus alpha)
  - clear comparison before vs. after
  - clear description in the report regarding your design choice  
e.g., why you chose the decision, why you cut the pipeline boundary, ....
  - report is VERY important

# Project Policy

- TA & Instructor **will not**
  - solve your project instead of you
  - debug your code (e.g., I got this error with screenshot, can you check my code ?)
  - analyze your issue (e.g., my performance is not so good, do you know why ?)
  - comment on your result (e.g., Can you check my result is correct ?, Can I get A grade with this optimization ?)
  - “fighting against errors” is the biggest part of this project
- However, TA & Instructor **will**
  - clarify the project problem
  - help any environment issue (e.g., it seems there is no license file, tool does not load, ...)
  - provide general guideline for a certain issue
- You can still discuss between students through discussion tab