

# **ECE260B Winter 22**



## **Low-power & High-performance Techniques**

**Prof. Mingu Kang**

**UCSD Computer Engineering**

# Clock gating

# CLK Gating with Glitch Risk

  



# Latch-based Clock Gating

- Clock Gating RTL Code

```
assign gclk = en && clk;
```

```
always @ (posedge clk) begin
    en <= XXXXX;
end
```
  
```
always @ (posedge gclk) begin
    out_q = in;
end
```




# Glitch-free Clock Gating

- Glitch-free Clock Gating

```
assign gclk = en_neg && clk;  
always @ (negedge clk) begin  
    en_neg <= XXXX;  
end
```

 
```
always @ (posedge gclk) begin  
    out_q <= in;  
end
```


 
# Instantiating CLK Gating Cell from STDcell


- Use of predefined clk gating cell

```
clkgate clkgate_instance .EN(enable), .CLK(clk), .GCLK(gclk);
```



# Pipelining

# Pipeline


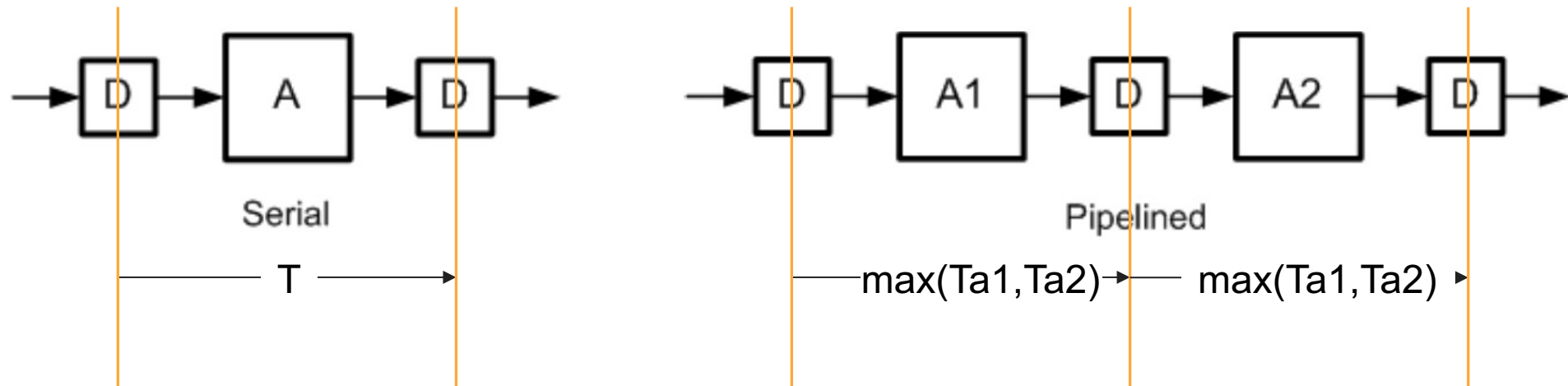


- Pipeline:



- divide the combinational logic path into multiple stages (above example: 2 stage pipeline)
- CLK period after pipeline:  $\max(T_{a1}, T_{a2}) < T$
- For uniform pipeline, ideally new CLK period can be  $T/2$ 
  - > 2X frequency up assuming no setup / hold time



# Pipeline in Different Cases

  


  Pipeline in the dataflow with two branches




Pipeline with the control signals
 
# Throughput and Latency in Pipelined System




before pipeline

 

after pipeline


cycle	1	2	3	4
①	$F(X_i)$	$F(X_{i+1})$	$F(X_{i+2})$	...
②	$Q(Y_i)$	$Q(Y_{i+1})$	$Q(Y_{i+2})$	...
③		$Z(F(X_i), Q(Y_i))$	$Z(F(X_{i+1}), Q(Y_{i+1}))$	...
 
# Throughput and Latency in Pipelined System



before pipeline

 
- Before pipeline
  - clk period: 43
  - Throughput:  $1/43$
  - Latency: 43




after pipeline

- After pipeline
  - clk period = 25
  - Throughput:  $1/25$
  - Latency:  $25 + 25 = 50$
  - assumption: ideal register  
e.g., no setup/hold time

# Further Pipeline

 



after pipeline

 

after more pipeline


- Further pipeline
  - If the target throughput / frequency hasn't met, apply further pipeline
  - Apply pipeline for slowest combination path
  - New throughput:  $1/18$ , New latency:  $18 * 3 = 54$

# Pipeline in Reality

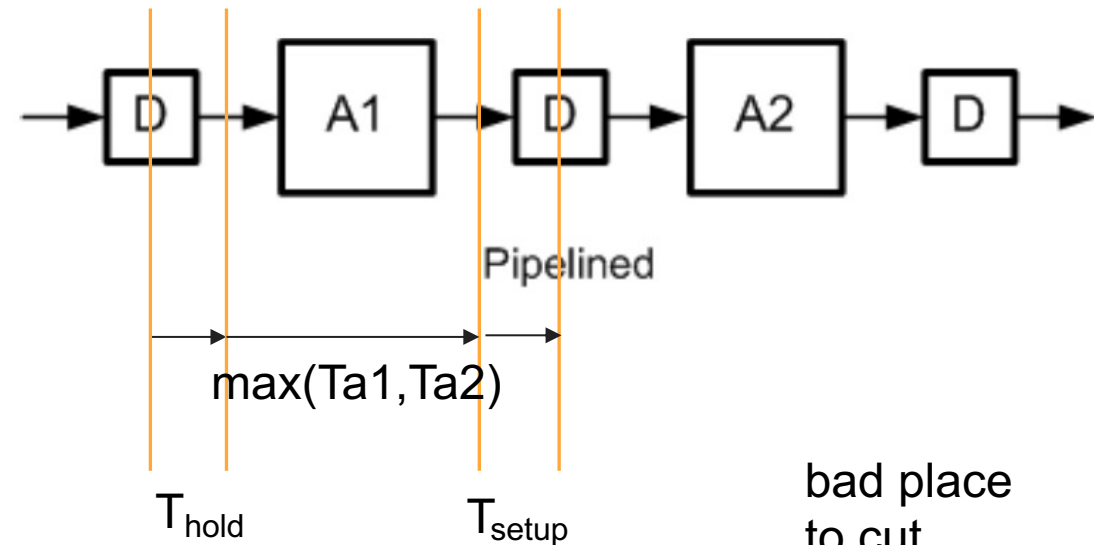
 


- Pipeline in reality:

 - Additional delay for  $T_{\text{hold}}$  and  $T_{\text{setup}}$
- Additional power / area consumption for registers
- Good to add pipeline registers at reduced paths




# Pipeline for Low-power

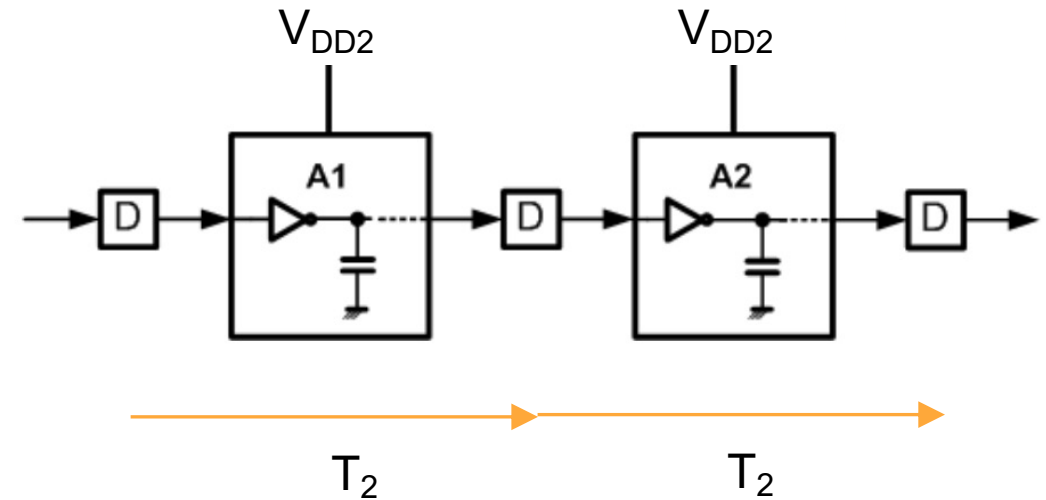 

- Pipeline for low  $V_{DD}$ :
  - $T_2 < T_1$  at same supply voltage ( $V_{DD1} = V_{DD2}$ )
  - To achieve the same frequency,  $V_{DD2}$  can be reduced by a factor of  $\alpha$
  - Power saving by a factor of  $\alpha^2$
 
# Pipeline in Cyclic Dataflow (Pipeline Hazard)



needs input  $x[n]$  and  $y[n-1]$ ,


but we do not have  $y[n-1]$  yet

cycle	1	2	3	4	5	...
s1	n	n+1	n+2	n+3		...
s2	n-1	n	n+1	n+2	n+3	...
s3	n-2	n-1	n	n+1	n+2	...
 
# Interleaving in Pipelined System

Two independent sets are interleaved

$x2[n+1]$   $x1[n+1]$   $x2[n+1]$   $x1[n+1]$   $x2[n]$   $x1[n]$   $\rightarrow$



needs input  $x[n]$  and  $y[n-1]$ ,

Now, we have  $y[n-1]$


cycle	1	2	3	4	5	...
s1	$n$	$n$	$n+1$	$n+1$		...
s2	$n-1$	$n$	$n$	$n+1$	$n+1$	...
s3	$n-1$	$n-1$	$n$	$n$	$n+1$	...



# Multi-path Design
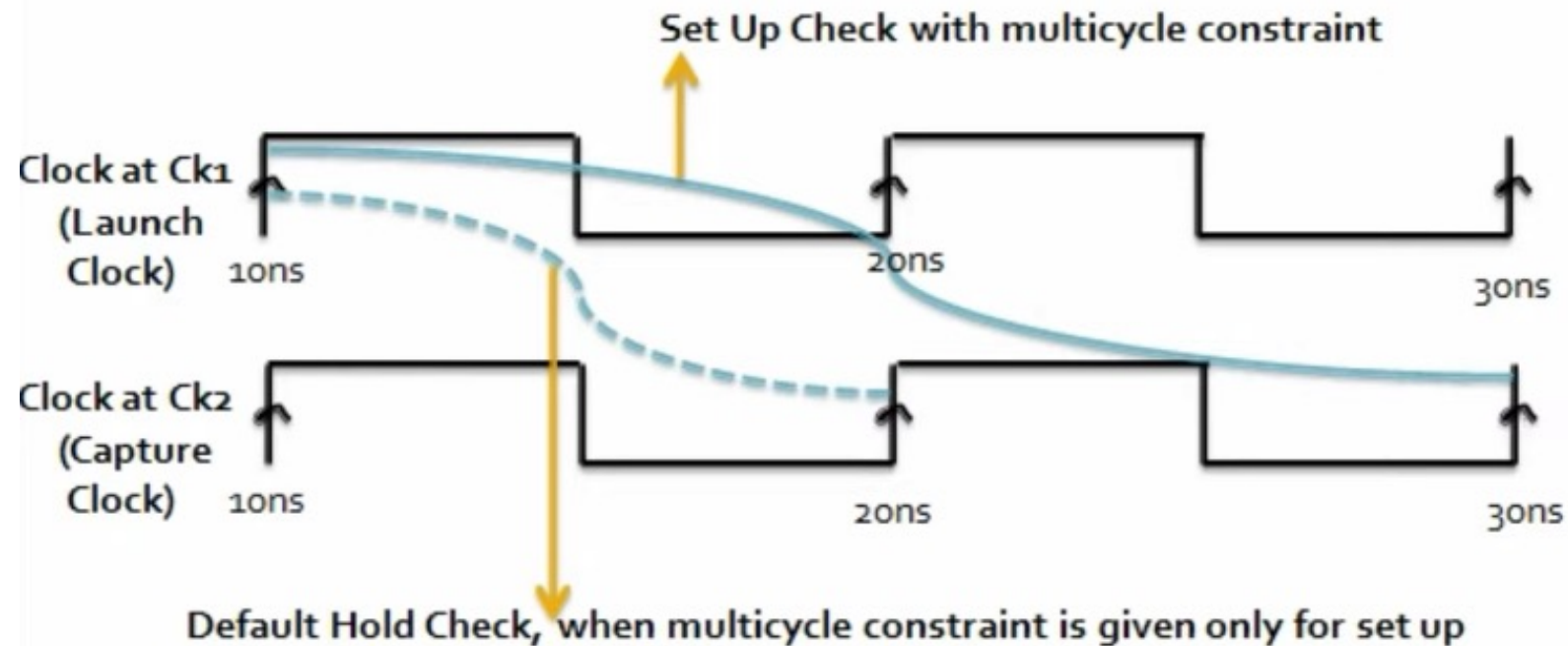
# Multicycle Setup without Hold Check

Set\_multicycle\_path -setup 2 -from FF1/Q -to FF2/D




# Multicycle Setup with Hold Check Correction

Set\_multicycle\_path -setup 2 -from FF1/Q -to FF2/D


Set\_multicycle\_path -hold 1 -from FF1/Q -to FF2/D

bring back hold timing by 1

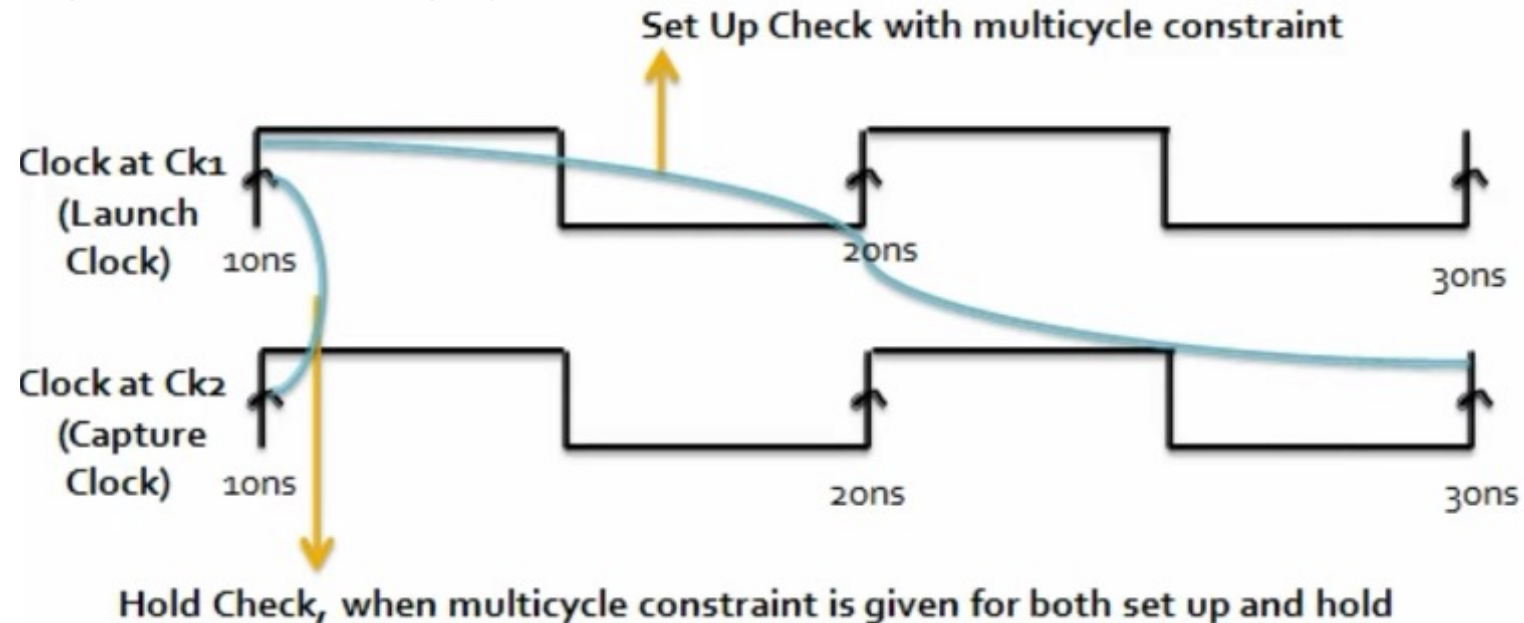



# Dynamic Voltage Frequency Scaling
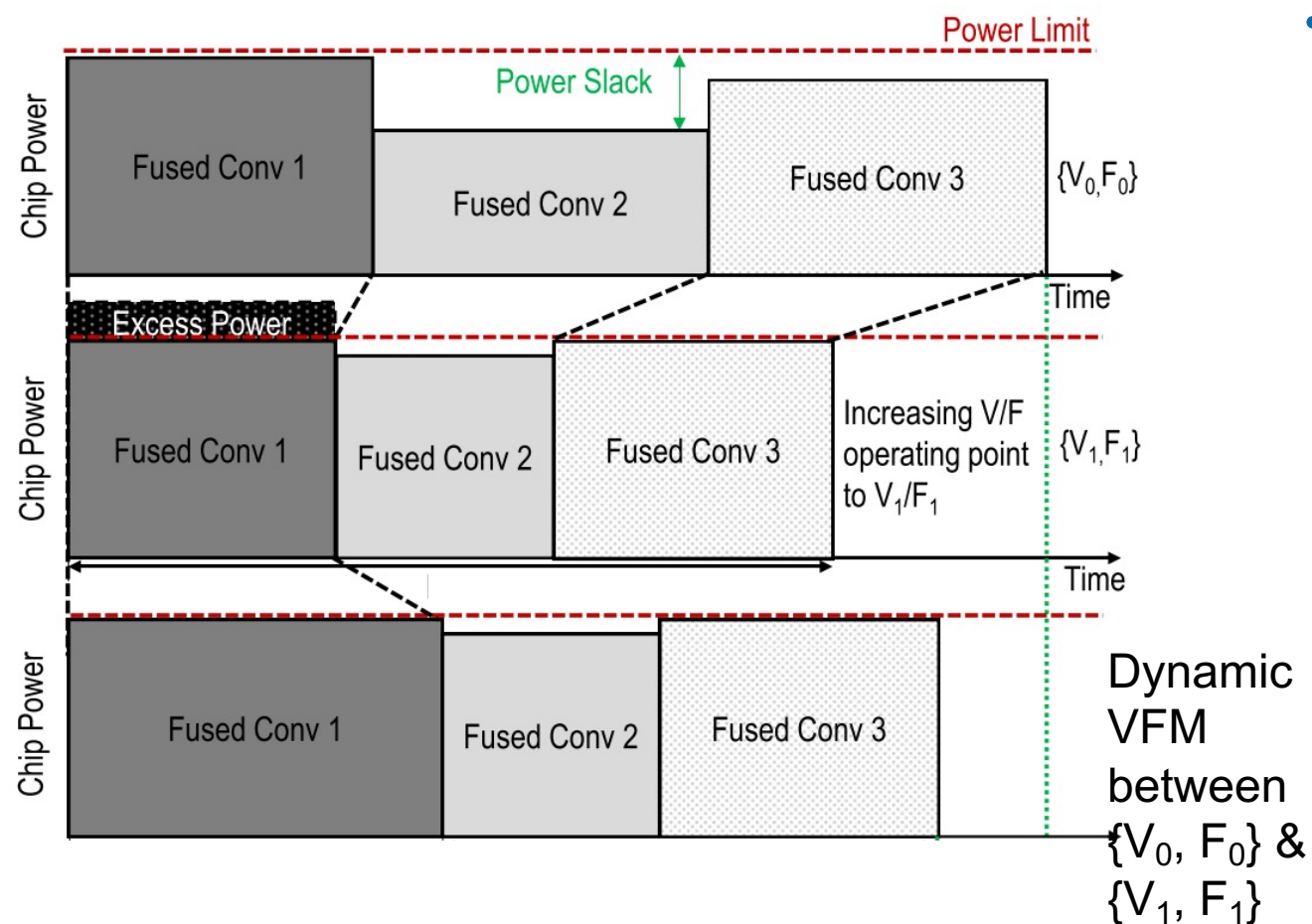
# DVFM (Dynamic Voltage Frequency Modulation)



- Dynamic frequency scaling
  - almost always appear with dynamic voltage scaling
  - known as **dynamic voltage and frequency scaling (DVFS)**.
  - when frequency is reduced, it is also called as “throttling”
  - used for power or heat management

# CLK Mux with Glitch Risk

  


Glitch

<https://vlsitutorials.com/glitch-free-clock-mux/>


# Glitch-free Clock Mux

“select” signal is 0

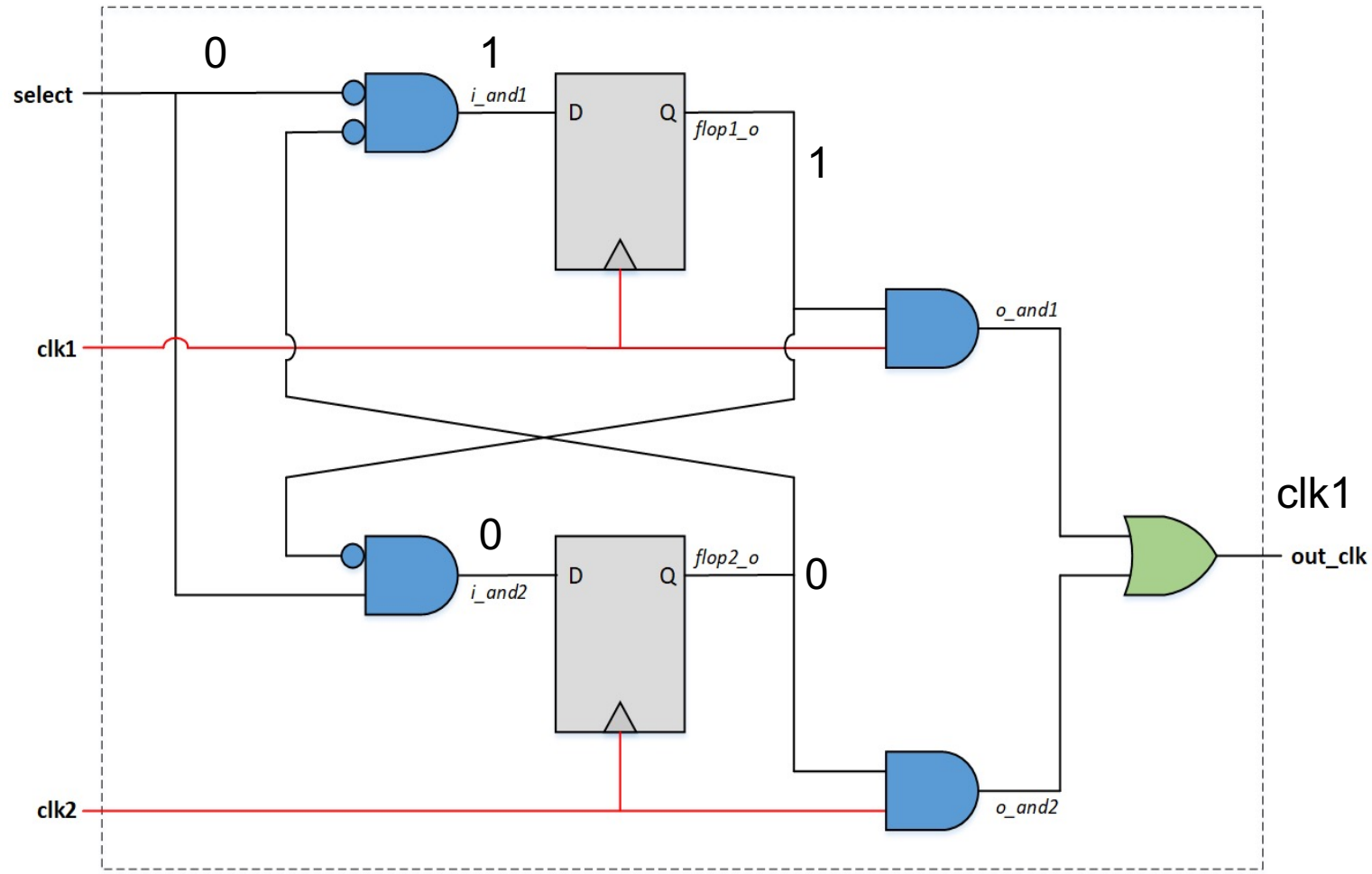
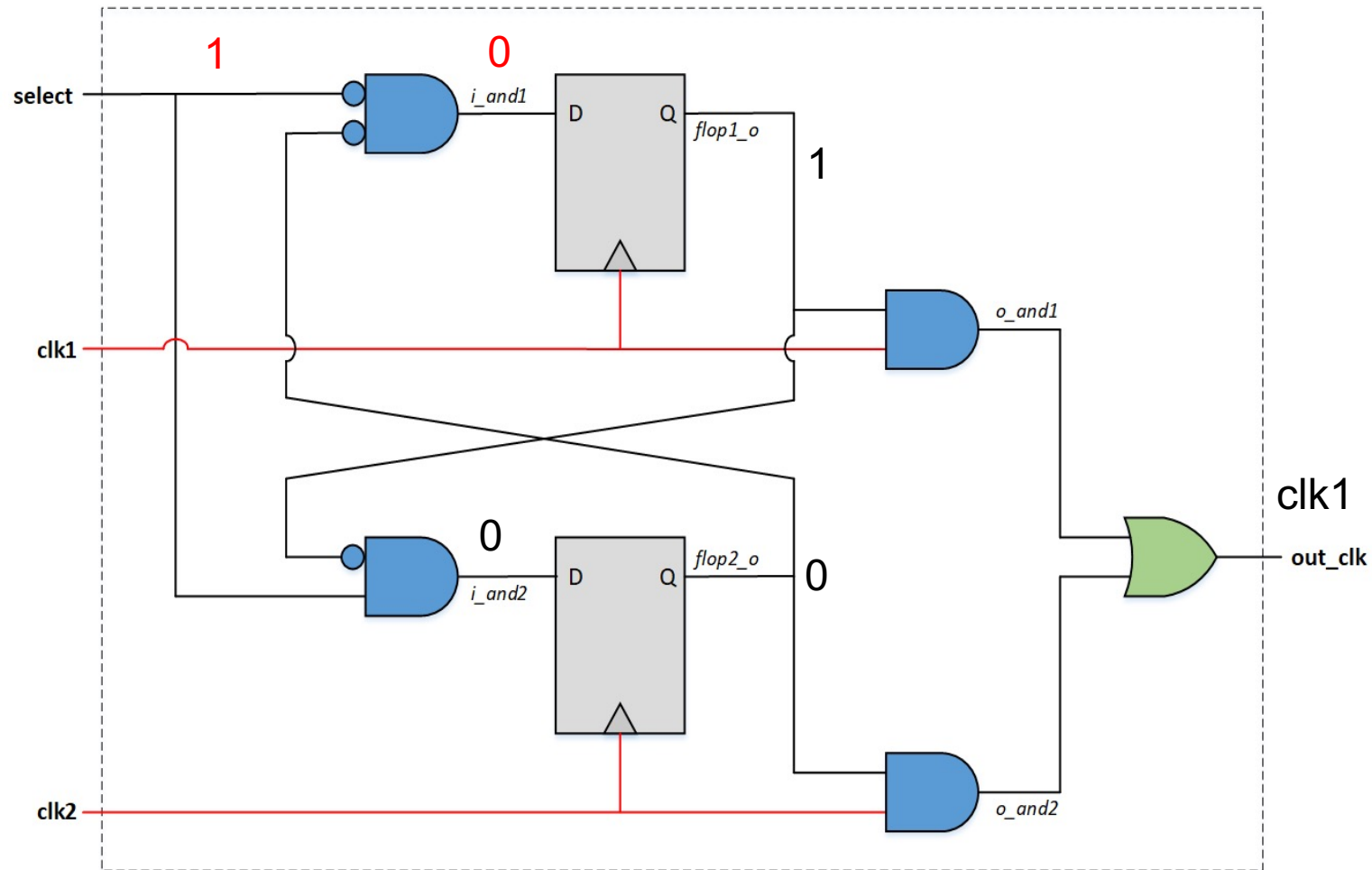
# Glitch-free Clock Mux


“select” changed:  
0 -> 1  
But clk rising edge  
hasn't come yet






# Glitch-free Clock Mux

clk rising edge  
has come

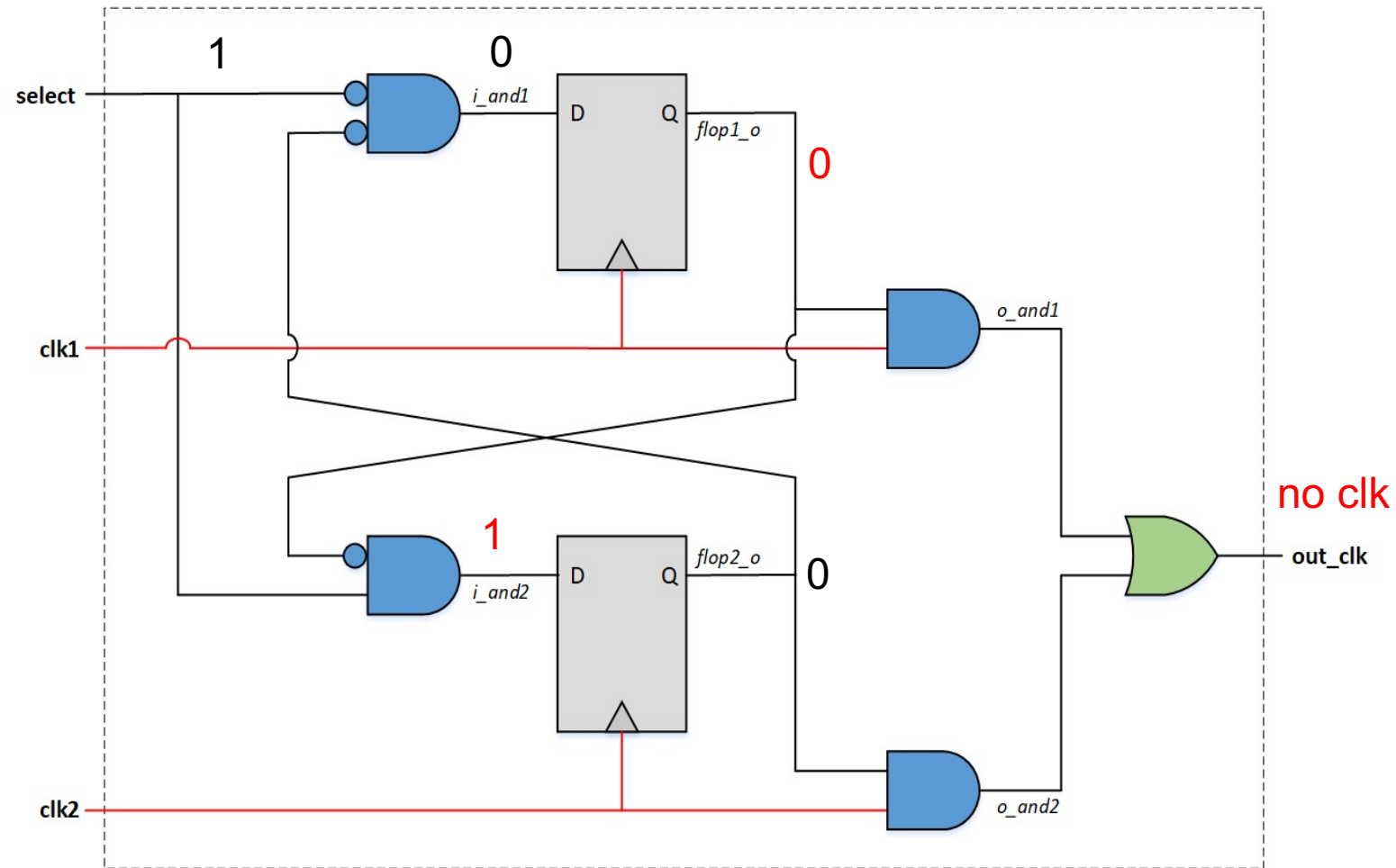


# Glitch-free Clock Mux

Another clk rising edge has come

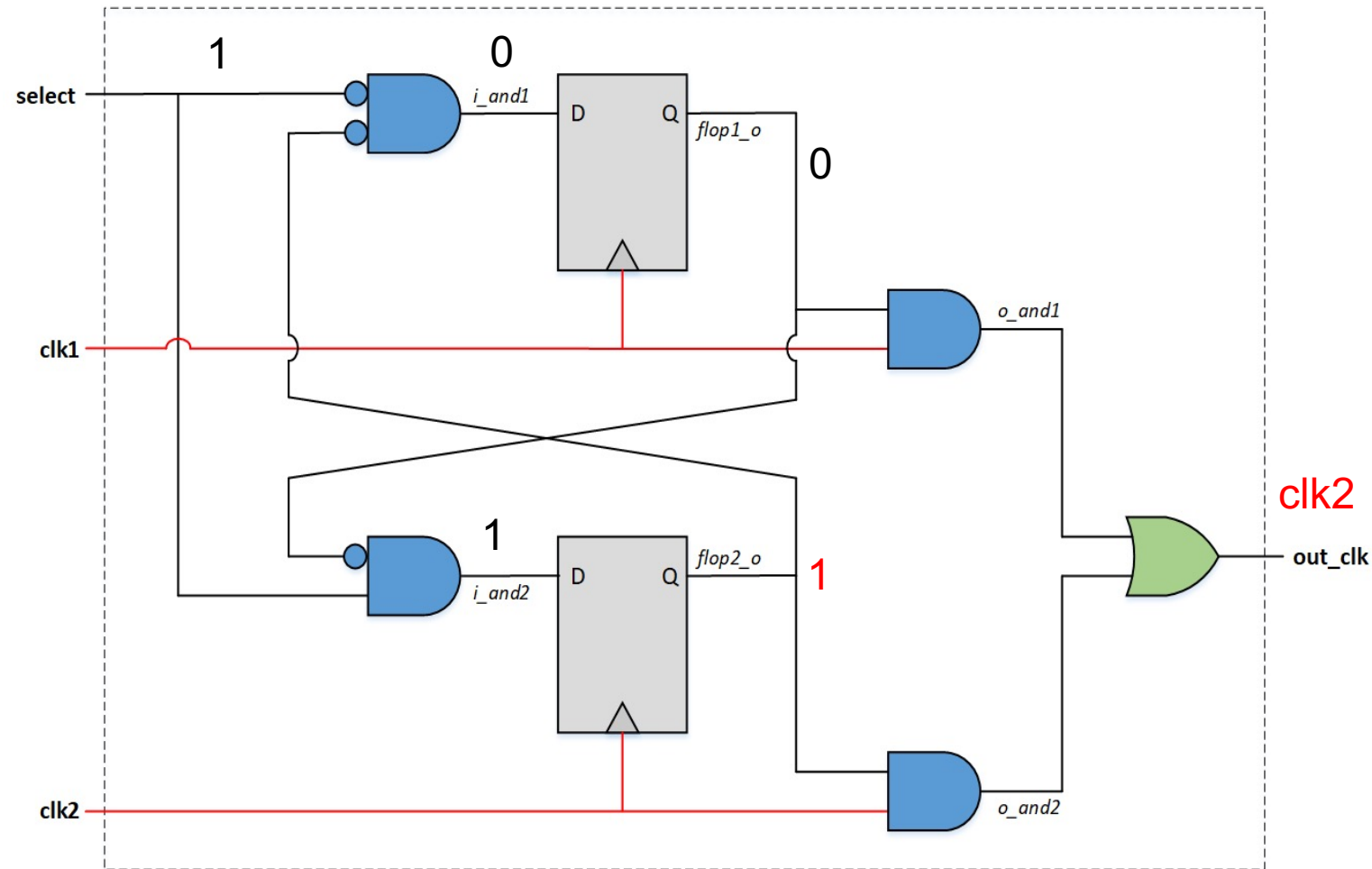

But, still there is an issue of asynchronous interface between `select` and `clk1` / `clk2`
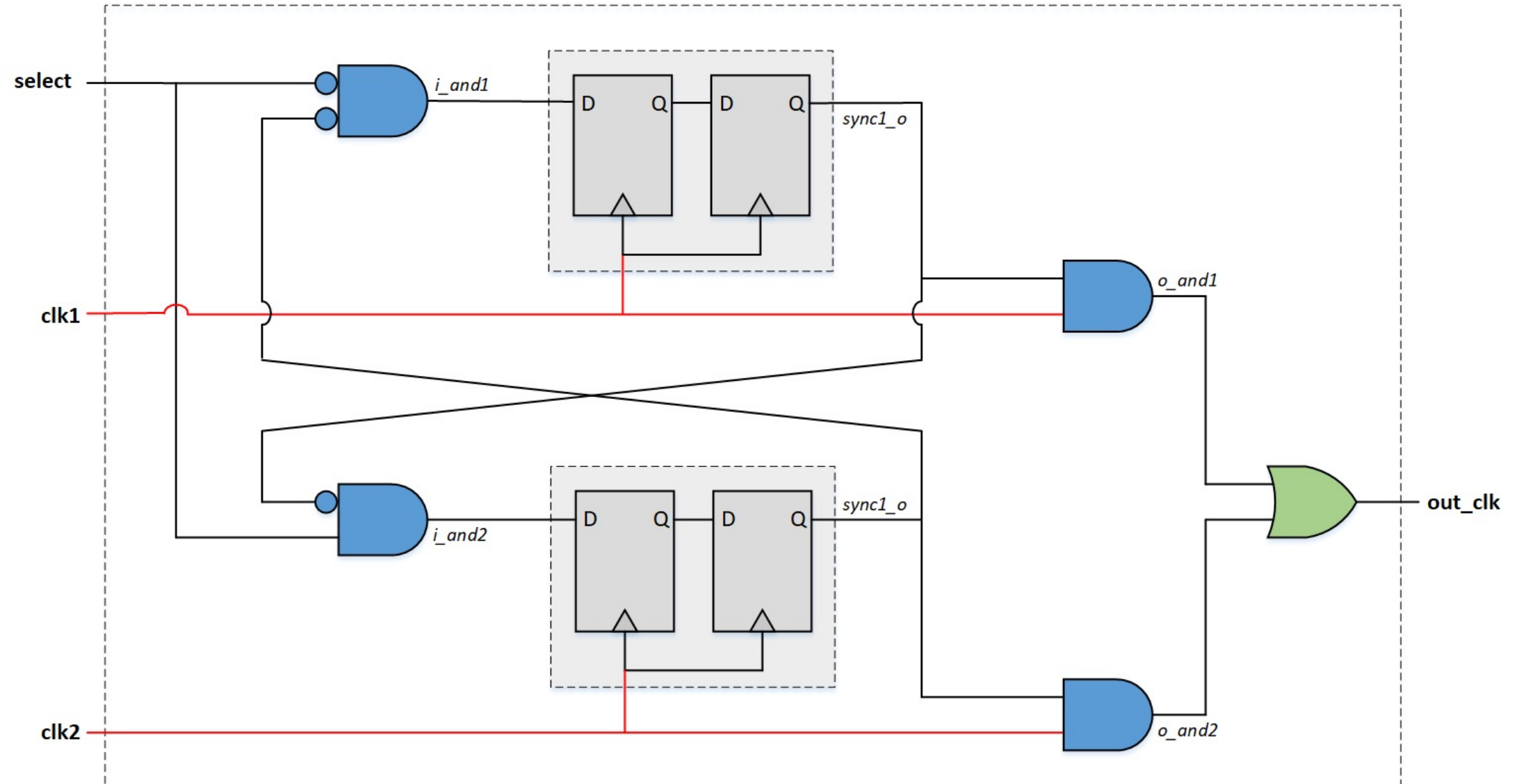
# Glitch-free Clock Mux with Synchronizer



# Loop Unrolling

# Loop Unrolling (Unfolding)

```
for (i = 0; i < N; i++) {  
    a[i]=b[i]*c[i];  
}
```


```
for (i = 0; i < N/2; i++) {  
    a[i*2] = b[i*2]*c[i*2];  
    a[i*2 + 1] = b[i*2 + 1]*c[i*2 + 1];  
}
```

- Loop unrolling
  - when there is some resource (time or area) budget, compute multiple terms in a single stage
  - frequency can be reduced with lower number of loop iterations
  - reduced loop management overhead, e.g., incrementing counter, checking condition
    - > potential power savings
  - opposite (folding) is also possible for frequency increase
 
# Hardware Example for Loop Unrolling

```
for (i=0; i<N; i++) {
    b[i] = a[i] + b[i]
}
```


```
for (i=0; i<N/4; i++) {
    b = a[4*i]+a[4*i+1]+a[4*i+2]+a[4*i+3]+b
}
```



# [HW] Pipeline of 16-tap Inner Product Computing

- 16 tap inner product computing with 8-bit for each operand
- e.g.,  $\text{out} = a[0]*b[0] + \dots a[15]*b[15]$
- Synthesis with typical corner targeting 1GHz freq with io\_delay 0.2 ns
- Measure the worst negative slack, area, and power
- Now, create a pipeline stage right after multiplication.
- Run the iverilog simulation to verify your pipelined version's functionality
- Synthesize again the pipelined version with the same condition
- Compare the worst negative slack, area, and power

# mac\_col.v

 

Inst[0]: K loading into register

Inst[1]: execute